 
 

Arithmetic-Logic Units (ALUs)



The four-bit adder


- The basic four-bit adder *always* computes $S = A + B + CI$



- But by changing what goes into the adder inputs A , B and CI , we can change the adder output S
- This is also what we did to build the combined adder-subtractor circuit


It's the adder-subtractor again!

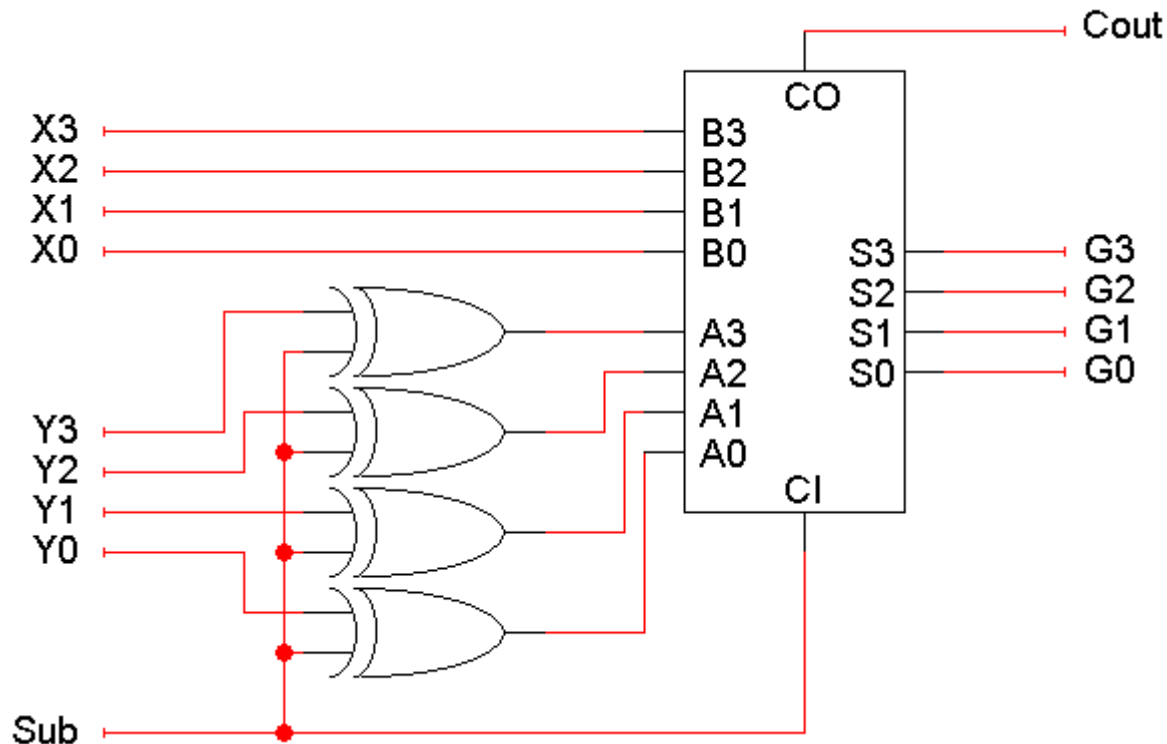- Here the signal Sub and some XOR gates alter the adder inputs
 - When **Sub = 0**, the adder inputs A, B, CI are $Y, X, 0$, so the adder produces $G = X + Y + 0$, or just $X + Y$
 - When **Sub = 1**, the adder inputs are Y', X and 1 , so the adder output is $G = X + Y' + 1$, or the two's complement operation $X - Y$




The multi-talented adder

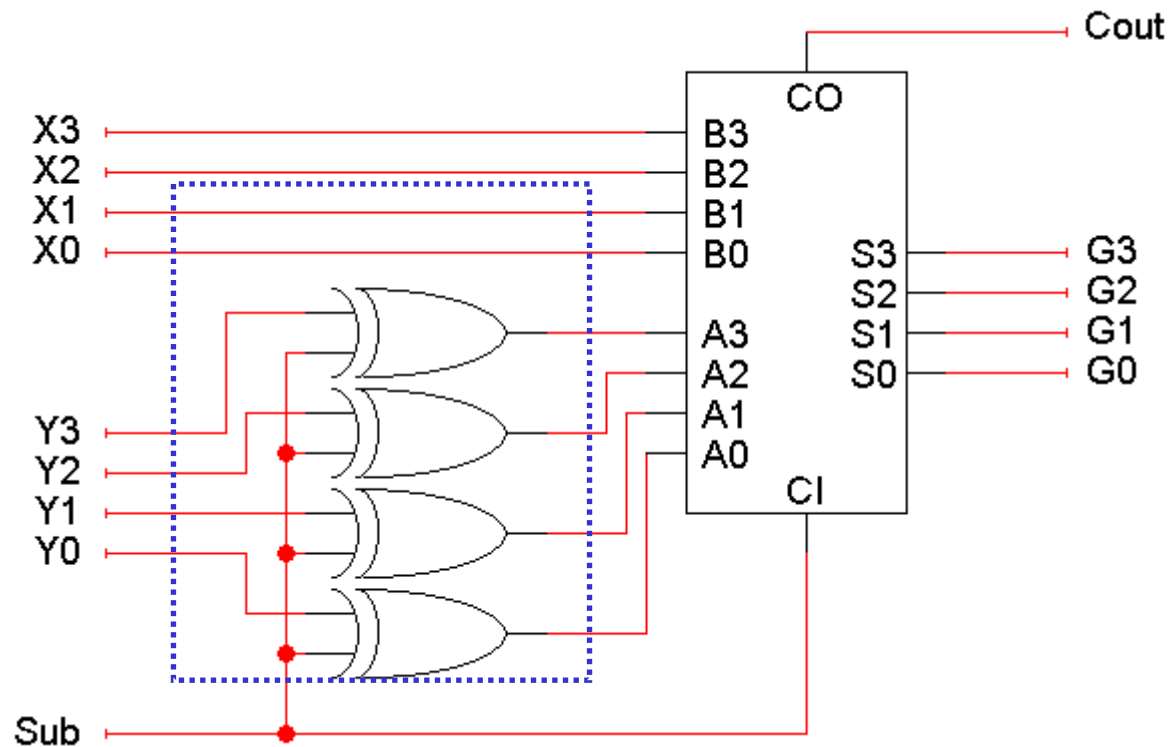- So we have one adder performing two separate functions
- "Sub" acts like a function select input which determines whether the circuit performs addition or subtraction
- Circuit-wise, all "Sub" does is modify the adder's inputs A and CI



Modifying the adder inputs

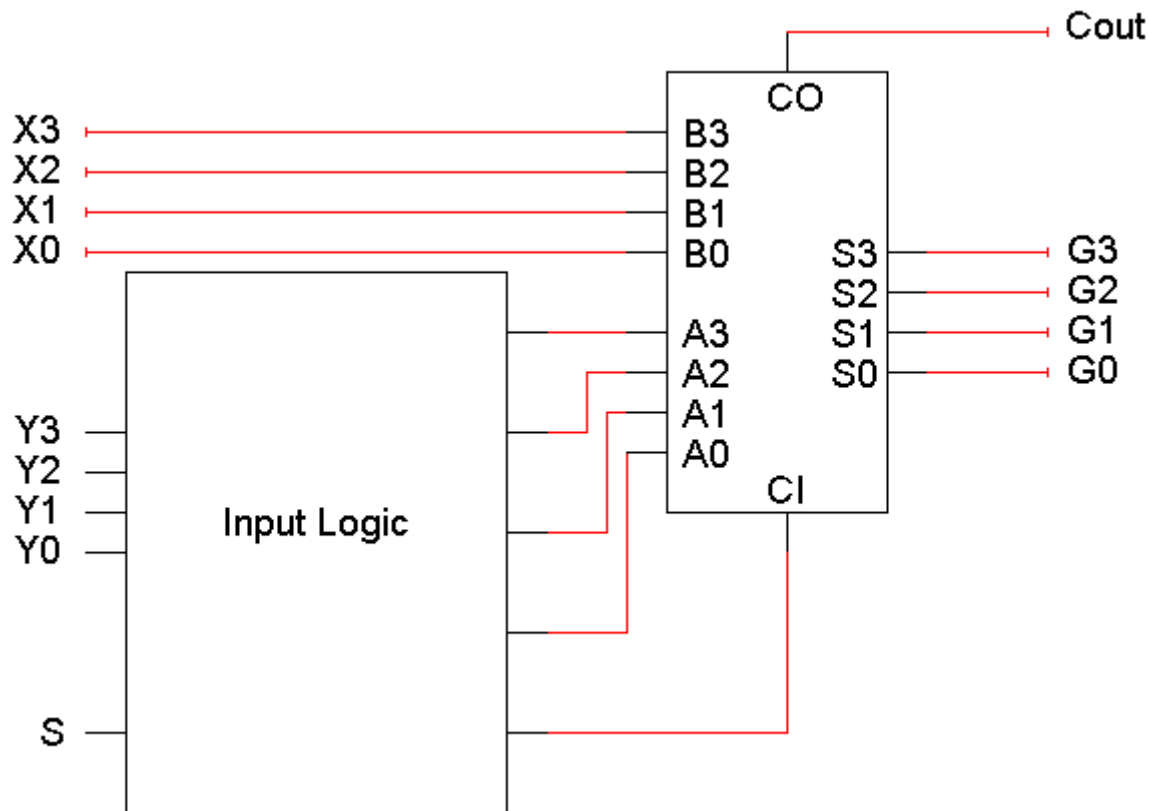- By following the same approach, we can use an adder to compute *other* functions as well
- We just have to figure out which functions we want, and then put the right circuitry into the "Input Logic" box



Some more possible functions

- We already saw how to set adder inputs A , B and CI to compute either $X + Y$ or $X - Y$
- How can we produce the increment function $G = X + 1$?

One way: Set $A = 0000$, $B = X$, and $CI = 1$

- How about decrement: $G = X - 1$?

$A = 1111$ (-1), $B = X$, $CI = 0$

- How about transfer: $G = X$?

$A = 0000$, $B = X$, $CI = 0$

This is almost the same as the increment function!

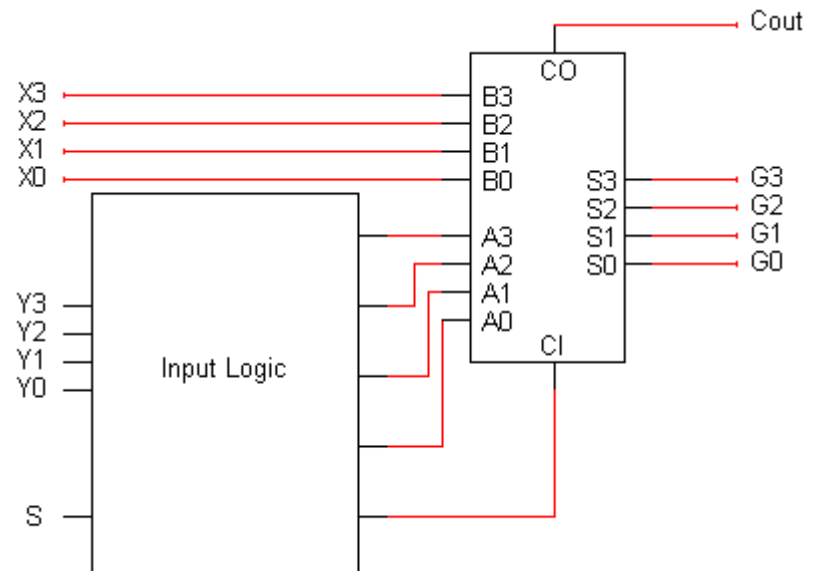


Table of arithmetic functions

- Here are some of the different possible arithmetic operations
- We'll need some way to specify which function we're interested in, so we've randomly assigned a selection code to each operation

| S_2 | S_1 | S_0 | Arithmetic operation | |
|-------|-------|-------|----------------------|------------------|
| 0 | 0 | 0 | X | (transfer) |
| 0 | 0 | 1 | $X + 1$ | (increment) |
| 0 | 1 | 0 | $X + Y$ | (add) |
| 0 | 1 | 1 | $X + Y + 1$ | |
| 1 | 0 | 0 | $X + Y'$ | (1C subtraction) |
| 1 | 0 | 1 | $X + Y' + 1$ | (2C subtraction) |
| 1 | 1 | 0 | $X - 1$ | (decrement) |
| 1 | 1 | 1 | X | (transfer) |

Mapping the table to an adder


- This second table shows what the adder's inputs should be for each of our eight desired arithmetic operations
 - Adder input CI is always the same as selection code bit S_0
 - B is always set to X
 - A depends only on S_2 and S_1
- These equations depend on both the desired operations and the assignment of selection codes

| Selection code | | | Desired arithmetic operation $G(A + B + CI)$ | Required adder inputs | | |
|----------------|-------|-------|---|-----------------------|-----|------|
| S_2 | S_1 | S_0 | | A | B | CI |
| 0 | 0 | 0 | X (transfer) | 0000 | X | 0 |
| 0 | 0 | 1 | $X + 1$ (increment) | 0000 | X | 1 |
| 0 | 1 | 0 | $X + Y$ (add) | Y | X | 0 |
| 0 | 1 | 1 | $X + Y + 1$ | Y | X | 1 |
| 1 | 0 | 0 | $X + Y'$ (1C subtraction) | Y' | X | 0 |
| 1 | 0 | 1 | $X + Y' + 1$ (2C subtraction) | Y' | X | 1 |
| 1 | 1 | 0 | $X - 1$ (decrement) | 1111 | X | 0 |
| 1 | 1 | 1 | X (transfer) | 1111 | X | 1 |

Building the input logic

- All we need to do is compute the adder input A , given the arithmetic unit input Y and the function select code S (actually just S_2 and S_1)
- Here is an abbreviated truth table:

| S_2 | S_1 | A |
|-------|-------|------|
| 0 | 0 | 0000 |
| 0 | 1 | Y |
| 1 | 0 | Y' |
| 1 | 1 | 1111 |

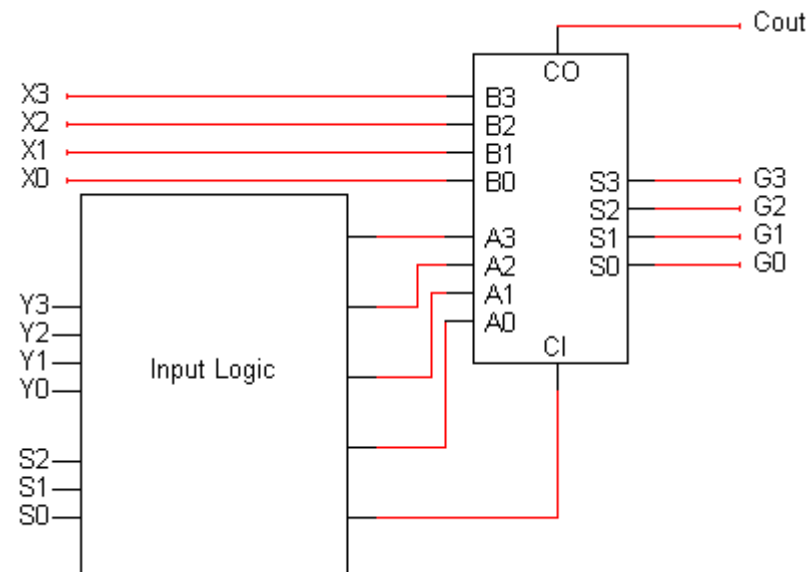


- We want to pick one of these four possible values for A , depending on S_2 and S_1

Primitive gate-based input logic

- We could build this circuit using primitive gates
- If we want to use K-maps for simplification, then we should first expand out the abbreviated truth table
 - The Y that appears in the output column (A) is actually an input
 - We make that explicit in the table on the right
- Remember A and Y are each 4 bits long!

| S_2 | S_1 | A |
|-------|-------|------|
| 0 | 0 | 0000 |
| 0 | 1 | Y |
| 1 | 0 | Y' |
| 1 | 1 | 1111 |

 

| S_2 | S_1 | Y_i | A_i |
|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |


Primitive gate implementation

- From the truth table, we can find an MSP:

| | | S ₁ | |
|----------------|---|----------------|---|
| S ₂ | 0 | 0 | 1 |
| | 1 | 0 | 1 |
| | | Y _i | |

$$A_i = S_2 Y_i' + S_1 Y_i$$

 - Again, we have to repeat this once for each bit Y₃-Y₀, connecting to the adder inputs A₃-A₀
- This completes our arithmetic unit



Bitwise operations

- Most computers also support logical operations like AND, OR and NOT, but extended to multi-bit **words** instead of just single bits
- To apply a logical operation to two words X and Y, apply the operation on each pair of bits X_i and Y_i :

$$\begin{array}{r} \text{AND} \quad \begin{array}{cccc} 1 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 \end{array} \\ \hline \begin{array}{cccc} 1 & 0 & 1 & 0 \end{array} \end{array}$$

$$\begin{array}{r} \text{OR} \quad \begin{array}{cccc} 1 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 \end{array} \\ \hline \begin{array}{cccc} 1 & 1 & 1 & 1 \end{array} \end{array}$$

$$\begin{array}{r} \text{XOR} \quad \begin{array}{cccc} 1 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 \end{array} \\ \hline \begin{array}{cccc} 0 & 1 & 0 & 1 \end{array} \end{array}$$


- We've already seen this informally in two's-complement arithmetic, when we talked about "complementing" all the bits in a number

Defining a logic unit

- A logic unit supports different logical functions on two multi-bit inputs X and Y , producing an output G
- This abbreviated table shows four possible functions and assigns a selection code S to each





| S_1 | S_0 | Output |
|-------|-------|------------------------|
| 0 | 0 | $G_i = X_i Y_i$ |
| 0 | 1 | $G_i = X_i + Y_i$ |
| 1 | 0 | $G_i = X_i \oplus Y_i$ |
| 1 | 1 | $G_i = X_i'$ |

 - We'll just use multiplexers and some primitive gates to implement this
- Again, we need one multiplexer for *each bit* of X and Y



Our simple logic unit

    - Inputs:
 - X (4 bits)
 - Y (4 bits)
 - S (2 bits)
- Outputs:
 - G (4 bits)




Our ALU function table

- This table shows a sample function table for an ALU
- All of the arithmetic operations have $S_3=0$, and all of the logical operations have $S_3=1$
- These are the same functions we saw when we built our arithmetic and logic units a few minutes ago
- Since our ALU only has 4 logical operations, we don't need S_2 . The operation done by the logic unit depends only on S_1 and S_0

| S_3 | S_2 | S_1 | S_0 | Operation |
|-------|-------|-------|-------|------------------------|
| 0 | 0 | 0 | 0 | $G = X$ |
| 0 | 0 | 0 | 1 | $G = X + 1$ |
| 0 | 0 | 1 | 0 | $G = X + Y$ |
| 0 | 0 | 1 | 1 | $G = X + Y + 1$ |
| 0 | 1 | 0 | 0 | $G = X + Y'$ |
| 0 | 1 | 0 | 1 | $G = X + Y' + 1$ |
| 0 | 1 | 1 | 0 | $G = X - 1$ |
| 0 | 1 | 1 | 1 | $G = X$ |
| 1 | x | 0 | 0 | $G = X \text{ and } Y$ |
| 1 | x | 0 | 1 | $G = X \text{ or } Y$ |
| 1 | x | 1 | 0 | $G = X \oplus Y$ |
| 1 | x | 1 | 1 | $G = X'$ |

A complete ALU circuit

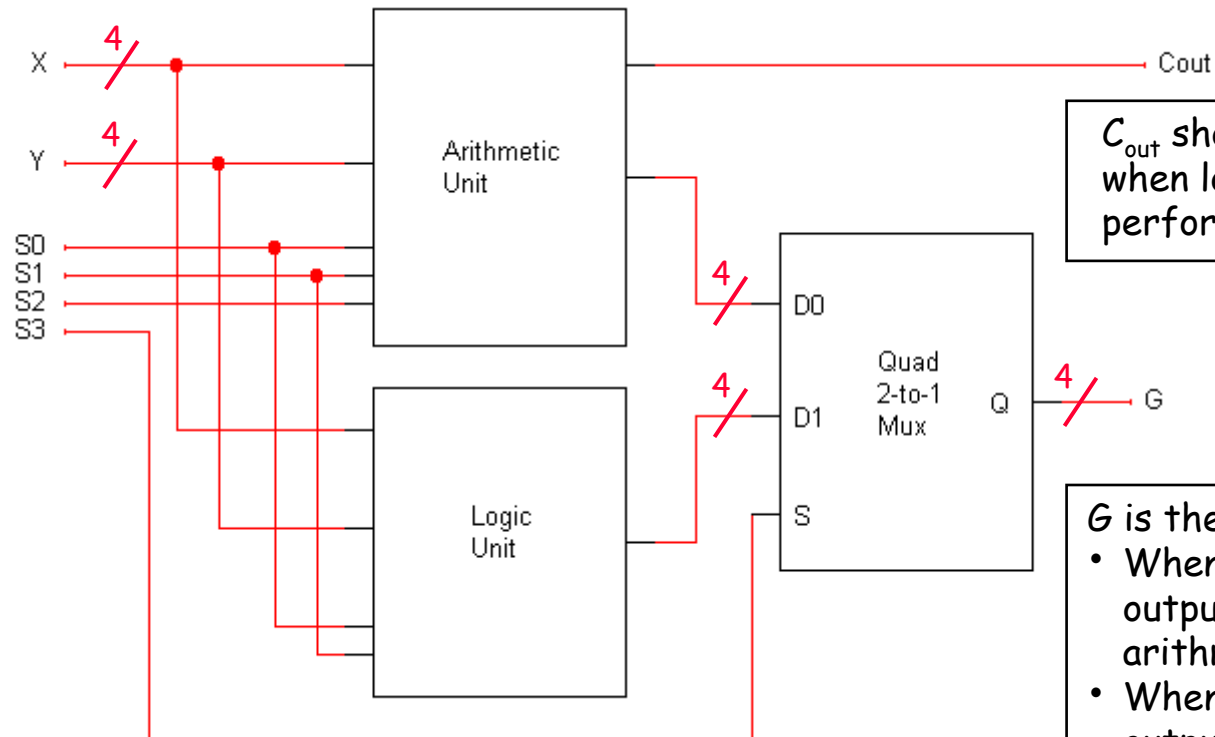The / and 4 on a line indicate that it's actually *four* lines.



C_{out} should be ignored when logic operations are performed (when $S3=1$).

G is the final ALU output.

- When $S3 = 0$, the final output comes from the arithmetic unit.
- When $S3 = 1$, the output comes from the logic unit.

The arithmetic and logic units share the select inputs $S1$ and $S0$, but only the arithmetic unit uses $S2$.

The completed ALU

- This ALU is a good example of hierarchical design
 - With the 12 inputs, the truth table would have had $2^{12} = 4096$ lines. That's an awful lot of paper.
 - Instead, we were able to use components that we've seen before to construct the entire circuit from a couple of easy-to-understand components
- As always, we encapsulate the complete circuit in a "black box" so we can reuse it in fancier circuits.

