

*CSE1003 Digital Logic and Design*  
*Module 4*  
*Combinational Circuits II*  
*L1*

---

DR. S.HEMAMALINI  
PROFESSOR  
SCHOOL OF ELECTRICAL ENGINEERING  
VIT CHENNAI

# Contents

6 hrs

---

Binary Parallel Adder - Look ahead carry

Magnitude Comparator

Decoders

Encoders

Multiplexers

Demultiplexers

CO4: Analyze the operation of medium complexity standard combinational circuits like the encoder, decoder multiplexer, demultiplexer.

# Applications – Magnitude Comparators


---

- ❖ Magnitude comparators are useful in control applications where a binary number representing the physical variable being controlled (e.g., position, speed, or temperature) is compared with a reference value. The comparator outputs are used to actuate circuitry to drive the physical variable toward the reference value.
- ❖ Comparators are used in central processing units (CPUs) and microcontrollers (MCUs).
- ❖ Comparators are also used as process controllers and for Servo motor control.
- ❖ Used in password verification and biometric applications.
 
# Magnitude Comparator

---

- ❑ The comparator is a  $2n$ -input, 3-output combinational logic circuit.
- ❑ It compares the magnitude of two  $n$ -bit numbers and provides the relative result as the output.



$$A = (A_{n-1}A_{n-2} \cdots A_0)_2$$

$$B = (B_{n-1}B_{n-2} \cdots B_0)_2$$

$$f_1 = 1, \quad \text{if } A < B$$

$$f_2 = 1, \quad \text{if } A = B$$

$$f_3 = 1, \quad \text{if } A > B$$

# 1-bit Magnitude Comparator

- The one-bit comparator is a combinational logic circuit with two inputs A and B and three outputs namely  $A < B$ ,  $A = B$  and  $A > B$ .
- It compares the two single bit numbers A and B and produces an output that indicates the result of the comparison.
- Let the 1-bit numbers be  $A = A_0$  and  $B = B_0$ .

## Design of 1-bit Magnitude Comparator

$$\begin{array}{c|cc} & A_0 & B_0 \\ & 0 & 1 \\ \hline B_0 & & \\ 0 & 0 & 0 \\ 1 & 1 & 0 \end{array}$$

K-map for  $A < B$

$$\begin{array}{c|cc} & A_0 & B_0 \\ & 0 & 1 \\ \hline B_0 & & \\ 0 & 1 & 0 \\ 1 & 0 & 1 \end{array}$$

K-map for  $A = B$

$$\begin{array}{c|cc} & A_0 & B_0 \\ & 0 & 1 \\ \hline B_0 & & \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{array}$$

K-map for  $A > B$

Truth table of a one-bit comparator

Inputs		Outputs		
A	B	$X(A < B)$	$Y(A = B)$	$Z(A > B)$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

For  $(A < B)$ ,

$$X = \overline{A_0} B_0$$


For  $(A = B)$ ,

$$Y = \overline{A_0} \overline{B_0} + A_0 B_0 = \overline{A_0 \oplus B_0}$$


For  $(A > B)$ ,

$$Z = A_0 \overline{B_0}$$

Logic diagram of 1-bit comparator

 

Using Basic Gates

 

Using AND and EX-NOR gates

# Design of 2-bit Magnitude Comparator

❑ A comparator used to compare two binary numbers each of two bits is called a 2-bit magnitude comparator.

❑ It consists of four inputs and three outputs to generate less than, equal to and greater than between two binary numbers.

❑ Let the two 2-bit binary numbers be  $A = A_1A_0$  and  $B = B_1B_0$ .

❑ Here each subscript represents one of the digits in the numbers.

❑ The binary numbers A and B will be equal if all the pairs of significant digits of both numbers are equal, i.e.,  $A_1 = B_1$  and  $A_0 = B_0$ .

Truth Table of 2-bit Magnitude Comparator

INPUT				OUTPUT		
A1	A0	B1	B0	A < B	A = B	A > B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

Procedure to compare 2 2bit binary numbers:

1. First compare the two most significant bits ( $A_1$  and  $B_1$ ).

If  $A_1 > B_1$ , then  $A > B$ ;

if  $A_1 < B_1$ , then  $A < B$ .

If  $A_1 = B_1$ , then the next pair of bits ( $A_0$  and  $B_0$ ) must be compared.

2. If  $A_1 = B_1$  and  $A_0 > B_0$ , then  $A > B$ ;

if  $A_1 = B_1$  and  $A_0 < B_0$ , then  $A < B$ .

Again, if  $A_1 = B_1$  and  $A_0 = B_0$ , then  $A = B$ .

# Design of 2-bit Magnitude Comparator

Truth Table of 2-bit Magnitude Comparator

INPUT				OUTPUT		
A1	A0	B1	B0	A < B	A = B	A > B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

A <sub>1</sub> A <sub>0</sub>	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00			1	1	1
01				1	1
11					
10				1	

For A < B

$$X = \overline{A_1}B_1 + \overline{A_1}B_0\overline{A_0} + \overline{A_0}B_1B_0$$

A <sub>1</sub> A <sub>0</sub>	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00		1			
01			1		
11				1	
10					1

For A = B

$$\begin{aligned}
 Y &= \overline{A_1}\overline{B_1}\overline{A_0}\overline{B_0} + \overline{A_1}A_0\overline{B_1}B_0 + A_1A_0B_1B_0 + A_1\overline{A_0}B_1\overline{B_0} \\
 &= \overline{A_1}\overline{B_1}(\overline{A_0}\overline{B_0} + A_0B_0) + A_1B_1(A_0B_0 + \overline{A_0}\overline{B_0}) \\
 &= \overline{A_1}\overline{B_1}(A_0 \odot B_0) + A_1B_1(A_0 \odot B_0) \\
 &= (A_0 \odot B_0)(\overline{A_1}\overline{B_1} + A_1B_1) \\
 &= (A_0 \odot B_0)(A_1 \odot B_1)
 \end{aligned}$$

A <sub>1</sub> A <sub>0</sub>	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00					
01		1			
11		1	1		1
10		1	1		

For A > B

$$Z = A_0\overline{B_1}\overline{B_0} + A_1A_0\overline{B_0} + A_1\overline{B_1}$$

## Design of 2-bit Magnitude Comparator

For A<B

$$X = \overline{A_1}B_1 + \overline{A_1}B_0\overline{A_0} + \overline{A_0}B_1B_0$$


For A=B

$$\begin{aligned} Y &= \overline{A_1}\overline{B_1}\overline{A_0}\overline{B_0} + \overline{A_1}A_0\overline{B_1}B_0 + A_1A_0B_1B_0 + A_1\overline{A_0}B_1\overline{B_0} \\ &= \overline{A_1}\overline{B_1}(\overline{A_0}\overline{B_0} + A_0B_0) + A_1B_1(A_0B_0 + \overline{A_0}\overline{B_0}) \\ &= \overline{A_1}\overline{B_1}(A_0 \odot B_0) + A_1B_1(A_0 \odot B_0) \\ &= (A_0 \odot B_0)(\overline{A_1}\overline{B_1} + A_1B_1) \\ &= (A_0 \odot B_0)(A_1 \odot B_1) \end{aligned}$$

For A>B

$$Z = A_0\overline{B_1}\overline{B_0} + A_1A_0\overline{B_0} + A_1\overline{B_1}$$

 Logic diagram of 2-bit Magnitude Comparator





# Design of 4-bit Magnitude Comparator

□ Let the two 4-bit numbers be  $A = A_3A_2A_1A_0$  and  $B = B_3B_2B_1B_0$

□ **Steps used in comparing two 4-bit numbers:**

1. First compare the two most significant bits ( $A_3$  and  $B_3$ ).

If  $A_3 > B_3$ , then  $A > B$ ; if  $A_3 < B_3$ , then  $A < B$ .

If  $A_3 = B_3$ , the next pair of bits ( $A_2$  and  $B_2$ ) must be compared.

2. If  $A_3 = B_3$  and  $A_2 > B_2$ , then  $A > B$ ;

if  $A_3 = B_3$  and  $A_2 < B_2$ , then  $A < B$

if  $A_3 = B_3$  and  $A_2 = B_2$ , the next pair of bits ( $A_1$  and  $B_1$ ) will be compared.

3. If  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 > B_1$ ; then  $A > B$ ;

if  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 < B_1$ , then  $A < B$ .

if  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 = B_1$ , compare the LSBs ( $A_0$  and  $B_0$ ).

4. If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$  and  $A_0 > B_0$ , then  $A > B$ ;

if  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$  and  $A_0 < B_0$ , then  $A < B$ .

5. If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$ ,  $A_0 = B_0$ , then  $A = B$ .

# Design of 4-bit Magnitude Comparator

A3B3	A2B2	A1B1	A0B0	A>B	A<B	A=B
A3>B3	x	x	x	1	0	0
A3<B3	x	x	x	0	1	0
A3=B3	A2>B2	x	x	1	0	0
A3=B3	A2<B2	x	x	0	1	0
A3=B3	A2=B2	A1>B1	x	1	0	0
A3=B3	A2=B2	A1<B1	x	0	1	0
A3=B3	A2=B2	A1=B1	A0>B0	1	0	0
A3=B3	A2=B2	A1=B1	A0<B0	0	1	0
A3=B3	A2=B2	A1=B1	A0=B0	0	0	1

The output A > B logic expression can be written as

$$G = A3 \overline{B3} + (A3 \text{ Ex-NOR } B3) A2 \overline{B2} + (A3 \text{ Ex-NOR } B3) (A2 \text{ Ex-NOR } B2) A1 \overline{B1} + (A3 \text{ Ex-NOR } B3) (A2 \text{ Ex-NOR } B2) (A1 \text{ Ex-NOR } B1) A0 \overline{B0}$$

The logical expression for A<B output can be written as

$$L = \overline{A3} B3 + (A3 \text{ Ex-NOR } B3) \overline{A2} B2 + (A3 \text{ Ex-NOR } B3) (A2 \text{ Ex-NOR } B2) \overline{A1} B1 + (A3 \text{ Ex-NOR } B3) (A2 \text{ Ex-NOR } B2) (A1 \text{ Ex-NOR } B1) \overline{A0} B0$$

The logical expression for A=B output can be written as

$$E = (A3 \text{ Ex-NOR } B3) (A2 \text{ Ex-NOR } B2) (A1 \text{ Ex-NOR } B1) (A0 \text{ Ex-NOR } B0)$$

## Design of 4-bit Magnitude Comparator

The output  $A > B$  logic expression can be written as


$$G = A_3 \overline{B_3} + (A_3 \text{ Ex-NOR } B_3) A_2 \overline{B_2} + (A_3 \text{ Ex-NOR } B_3) (A_2 \text{ Ex-NOR } B_2) A_1 \overline{B_1} + (A_3 \text{ Ex-NOR } B_3) (A_2 \text{ Ex-NOR } B_2) (A_1 \text{ Ex-NOR } B_1) A_0 \overline{B_0}$$

The logical expression for  $A < B$  output can be written as

$$L = \overline{A_3} B_3 + (A_3 \text{ Ex-NOR } B_3) \overline{A_2} B_2 + (A_3 \text{ Ex-NOR } B_3) (A_2 \text{ Ex-NOR } B_2) \overline{A_1} B_1 + (A_3 \text{ Ex-NOR } B_3) (A_2 \text{ Ex-NOR } B_2) (A_1 \text{ Ex-NOR } B_1) \overline{A_0} B_0$$

The logical expression for  $A = B$  output can be written as

 
$$E = (A_3 \text{ Ex-NOR } B_3) (A_2 \text{ Ex-NOR } B_2) (A_1 \text{ Ex-NOR } B_1) (A_0 \text{ Ex-NOR } B_0)$$




Logic diagram of 4-bit Comparator
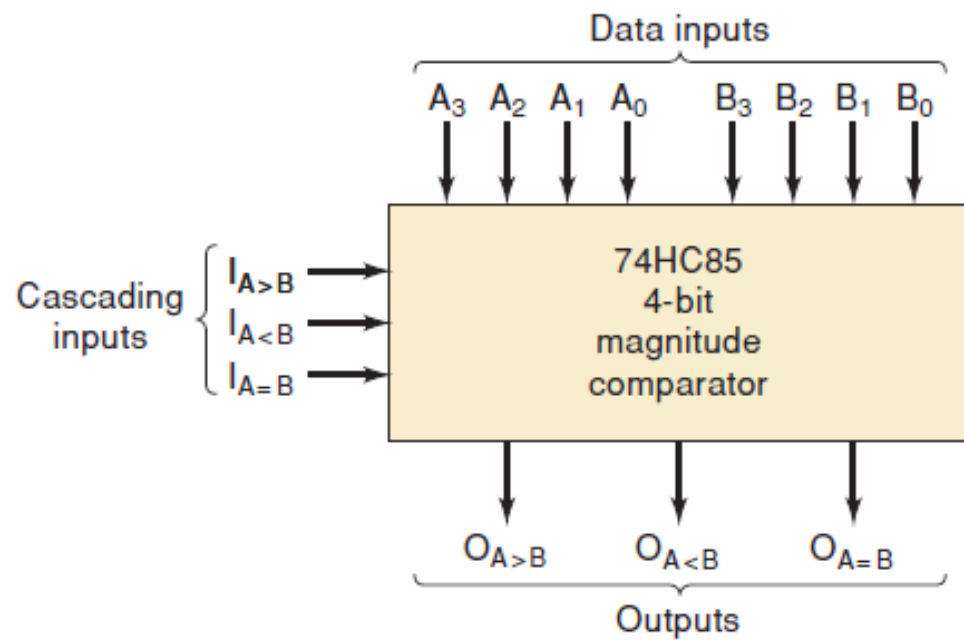
# MAGNITUDE COMPARATOR

- ❑ Magnitude Comparators are available in IC form.
- ❑ 7485 is a 4-bit magnitude comparator of the TTL logic family.



**Logic Symbol**

 

**Pin Configuration**

## Data Inputs

$$A = (A_3, A_2, A_1, A_0)_2$$

$$B = (B_3, B_2, B_1, B_0)_2$$

## Cascade Inputs

$$C1 \rightarrow A < B$$

$$C2 \rightarrow A = B$$

$$C3 \rightarrow A > B$$

## Outputs

$$O_{A<B}$$

$$O_{A>B}$$

$$O_{A=B}$$

Cascading inputs provide a means for expanding the comparison operation to more than four bits by cascading two or more four-bit comparators.

# MAGNITUDE COMPARATOR

TRUTH TABLE


COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
$A_3, B_3$	$A_2, B_2$	$A_1, B_1$	$A_0, B_0$	$I_{A>B}$	$I_{A<B}$	$I_{A=B}$	$O_{A>B}$	$O_{A<B}$	$O_{A=B}$
$A_3 > B_3$	X	X	X	X	X	X	H	L	L
$A_3 < B_3$	X	X	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 > B_2$	X	X	X	X	X	H	L	L
$A_3 = B_3$	$A_2 < B_2$	X	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	X	X	X	X	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	X	X	X	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	H	L	L	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	H	L	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	X	X	H	L	L	H
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	L	L	H	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	H	H	L	L	L	L

H = HIGH Voltage Level


L = LOW Voltage Level

X = Immaterial

# MAGNITUDE COMPARATOR

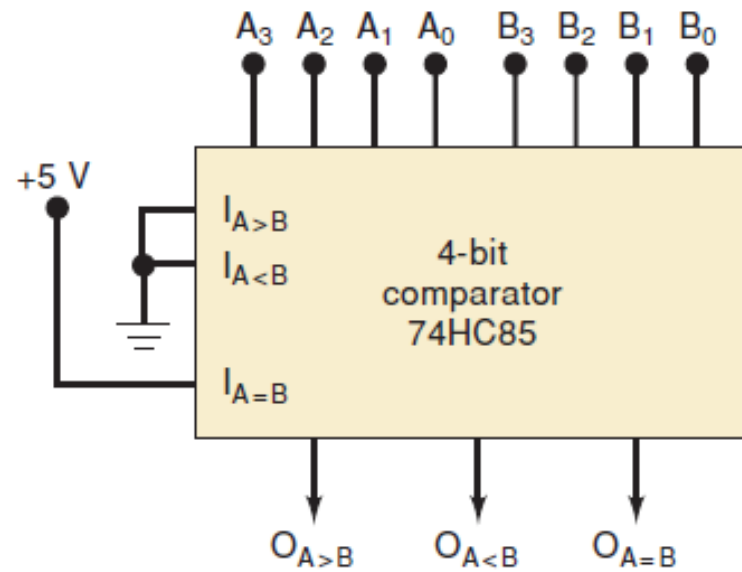

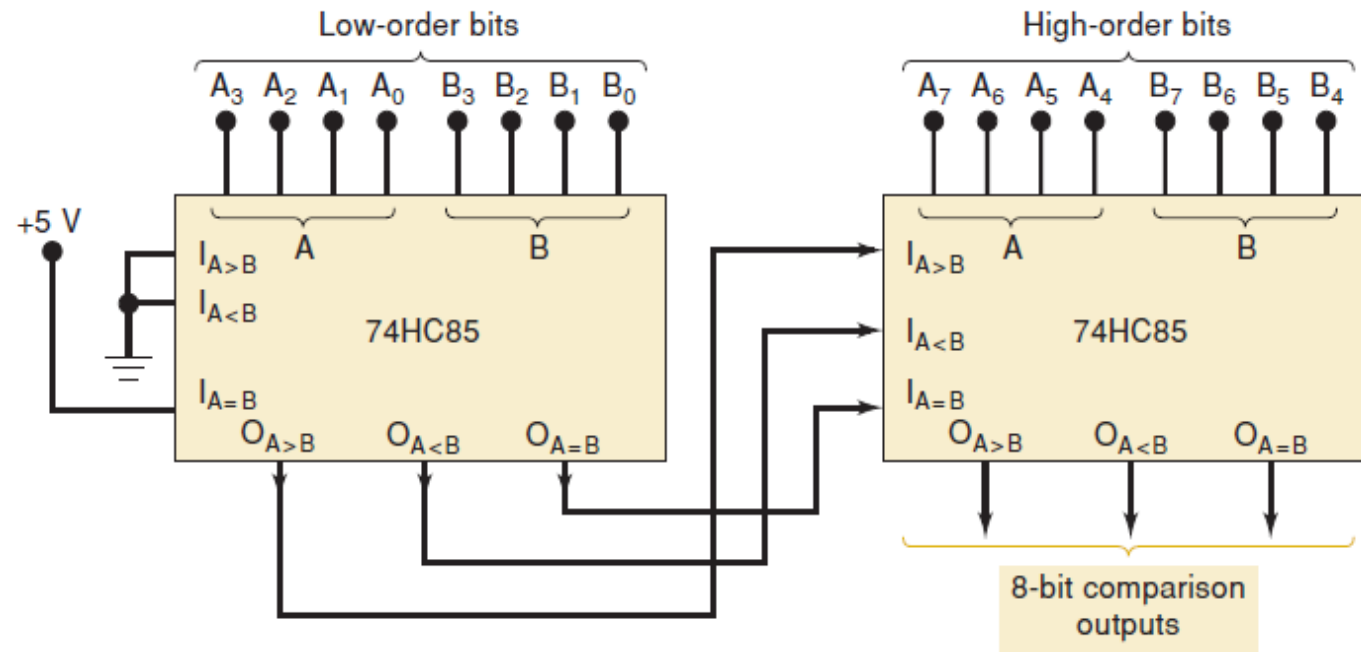(a) 74HC85 wired as a four-bit comparator



(b) Two 74HC85s cascaded to perform an eight-bit comparison

# MAGNITUDE COMPARATOR

Describe the operation of the eight-bit comparison arrangement in Figure for the following cases:


(a)  $A_7A_6A_5A_4A_3A_2A_1A_0 = 10101111$ ;  $B_7B_6B_5B_4B_3B_2B_1B_0 = 10110001$

(b)  $A_7A_6A_5A_4A_3A_2A_1A_0 = 10101111$ ;  $B_7B_6B_5B_4B_3B_2B_1B_0 = 10101001$

Solution:

a)  $O_{A<B}=1$

b)  $O_{A>B}=1$

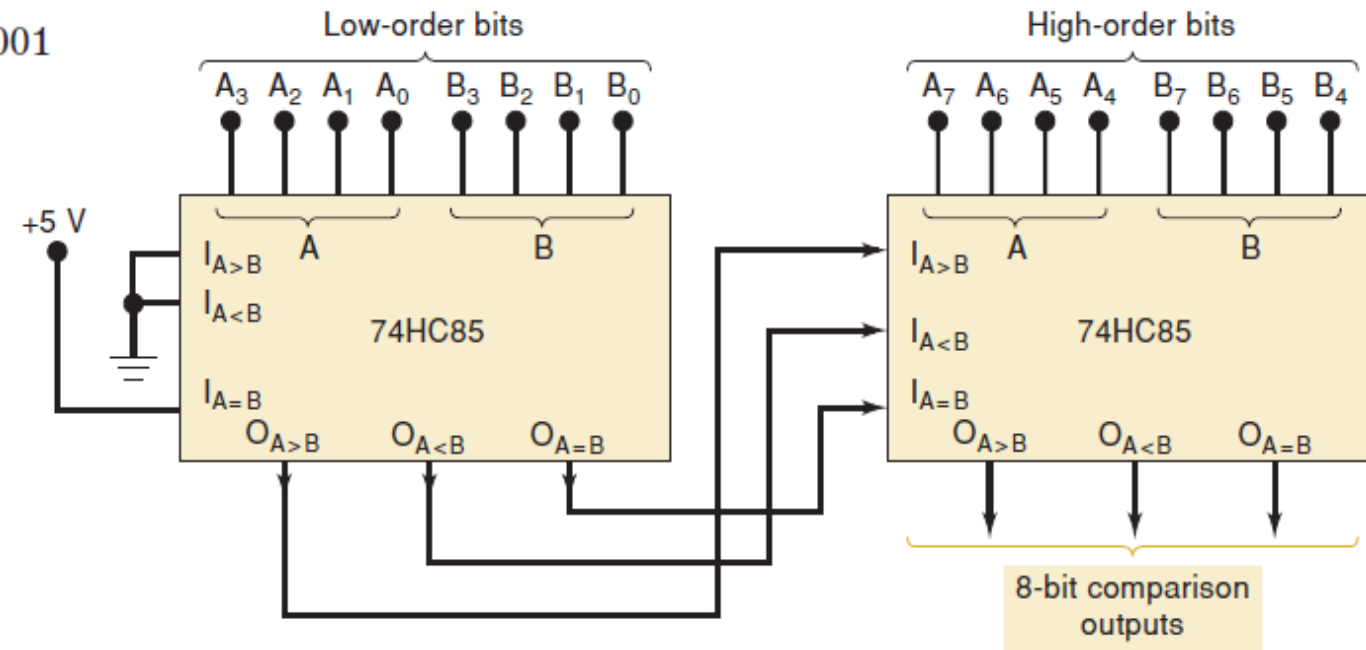

Design a 5-bit comparator using a single 7485 and one gate.

The two 5-bit numbers to be compared are

$X_4 X_3 X_2 X_1 X_0$  and  $Y_4 Y_3 Y_2 Y_1 Y_0$

