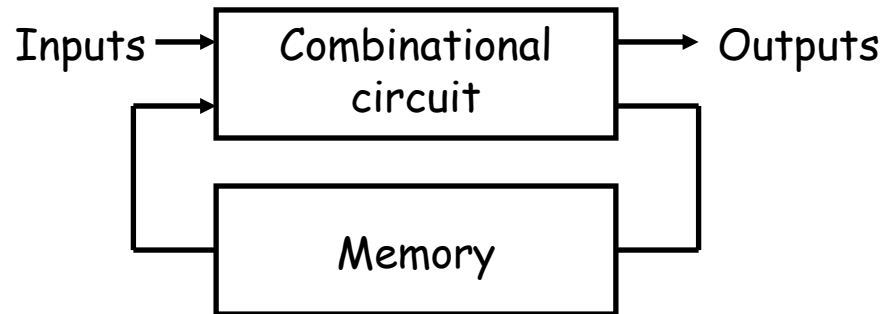
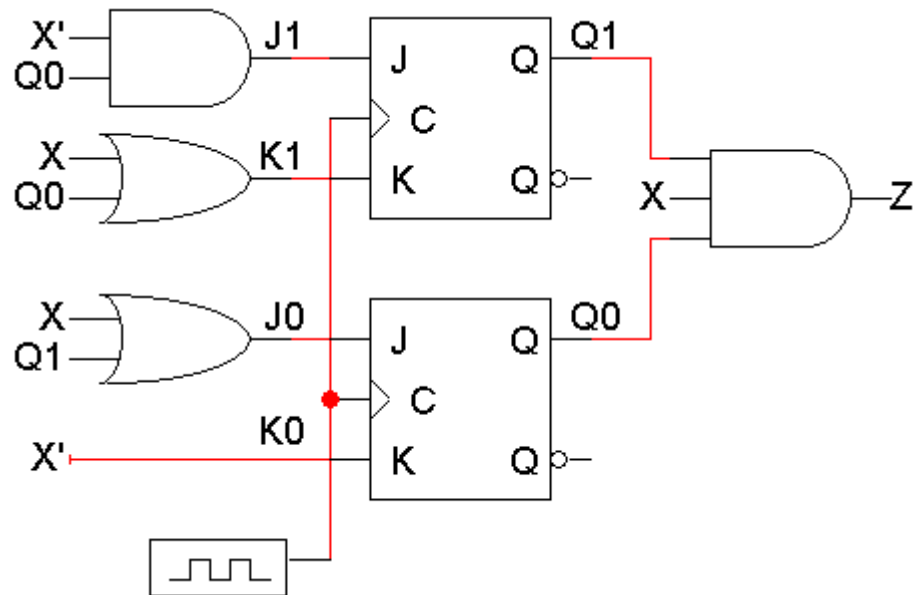

Sequential Circuit Analysis

Mealy or Moore???

- The output of a sequential circuit can be expressed in two different ways:
 - **Moore model:** Outputs= $f(\text{present state})$
 - **Mealy model:** Outputs: $f(\text{present state, inputs})$



An example sequential circuit




- A sequential circuit with two JK flip-flops
- **State or memory:** $Q1Q0$
- One input: X ; One output: Z

How do you describe a sequential circuit?

- A combinational circuit - Truth table, which shows how the outputs are related to the inputs
- A sequential circuit - **State table**, which shows inputs *and* current states on the left, and outputs *and* next states on the right
 - Need to find the next state of the FFs based on the present state and inputs
 - Need to find the output of the circuit as a function of
 - › current state for a circuit of the Moore model
 - › current state and inputs for a circuit of the Mealy model

State table of example circuit

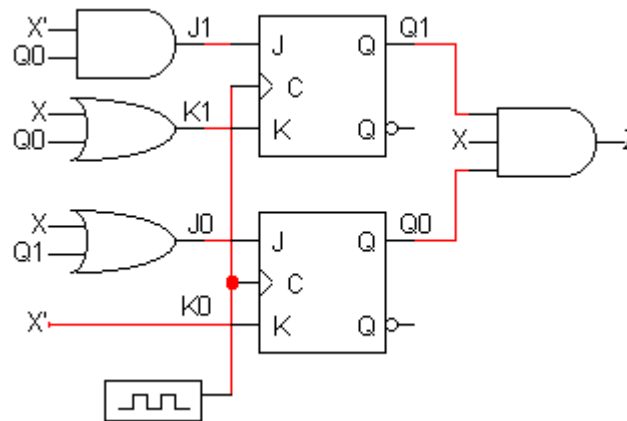


Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

The outputs are easy

- From the diagram, you can see that

$$Z = Q_1 Q_0 X$$

Mealy model circuit !!!

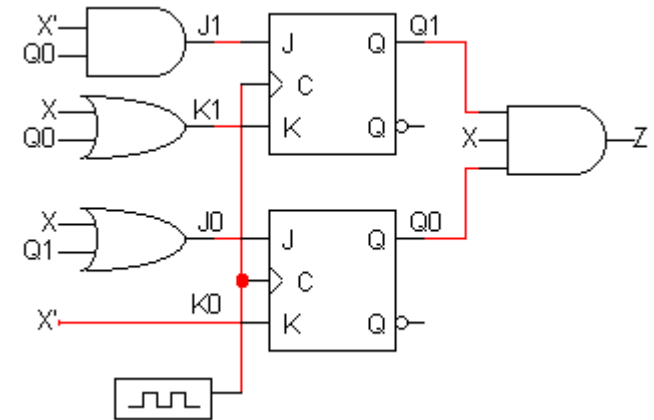

Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0			0
0	0	1			0
0	1	0			0
0	1	1			0
1	0	0			0
1	0	1			0
1	1	0			0
1	1	1			1

Flip-flop input equations

- Finding the next states is harder

Step 1:

Find Boolean expressions for the flip-flop inputs
i.e., How do the inputs (say, J & K) to the flip-flops
depend on the current state and input

Step 2:

Use these expressions to find the actual flip-flop input values for
each possible combination of present states and inputs
i.e., Fill in the state table (with new intermediate columns)

Step 3:

Use flip-flop characteristic tables or equations to find the next
states, based on the flip-flop input values and the present states

Step 1: Flip-flop input equations


- For our example, the flip-flop input equations are:

$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

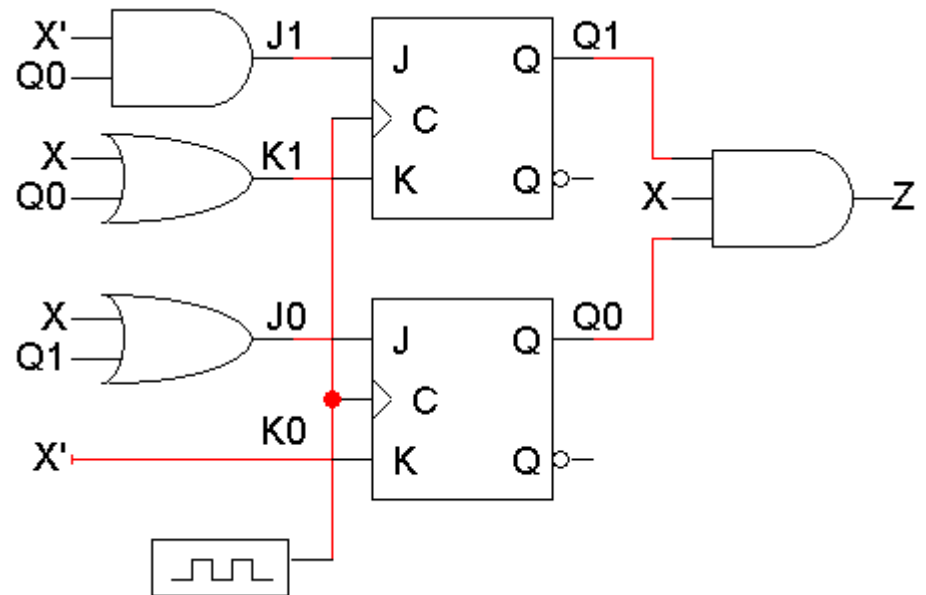

Step 2: Flip-flop input values

- With these equations, we can make a table showing J_1 , K_1 , J_0 and K_0 for the different combinations of present state Q_1Q_0 and input X

$$J_1 = X' Q_0$$


$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

Present State		Inputs	Flip-flop Inputs			
Q_1	Q_0	X	J_1	K_1	J_0	K_0
0	0	0	0	0	0	1
0	0	1	0	1	1	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
1	0	0	0	0	1	1
1	0	1	0	1	1	0
1	1	0	1	1	1	1
1	1	1	0	1	1	0

Step 2: Flip-flop input values

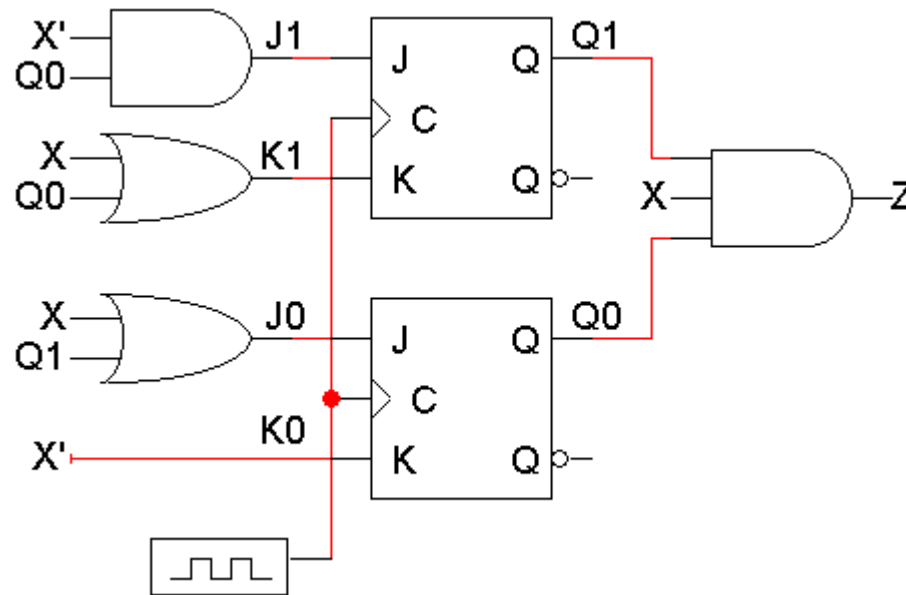

Present State		Inputs X	Flip-flop Inputs			
Q_1	Q_0		J_1	K_1	J_0	K_0
0	0	0	0	0	0	1
0	0	1	0	1	1	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
1	0	0	0	0	1	1
1	0	1	0	1	1	0
1	1	0	1	1	1	1
1	1	1	0	1	1	0

Step 3: Find the next states

- Finally, use the JK flip-flop characteristic tables or equations to find the next state of *each* flip-flop, based on its present state and inputs
- The general JK flip-flop characteristic equation is:

$$Q(t+1) = K'Q(t) + JQ'(t)$$

- In our example circuit, we have two JK flip-flops, so we have to apply this equation to *each* of them:

$$Q_1(t+1) = K_1'Q_1(t) + J_1Q_1'(t)$$

$$Q_0(t+1) = K_0'Q_0(t) + J_0Q_0'(t)$$

- We can also determine the next state for each input/current state combination directly from the characteristic table

J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Step 3 concluded

- The next states for Q_1 and Q_0 , are calculated using these equations:

$$\longrightarrow Q_1(t+1) = K_1'Q_1(t) + J_1Q_1'(t)$$

$$Q_0(t+1) = K_0'Q_0(t) + J_0Q_0'(t)$$

Present State		Inputs X	FF Inputs				Next State	
Q_1	Q_0		J_1	K_1	J_0	K_0	Q_1	Q_0
0	0	0	0	0	0	1		
0	0	1	0	1	1	0		
0	1	0	1	1	0	1	1	
0	1	1	0	1	1	0		
1	0	0	0	0	1	1		
1	0	1	0	1	1	0		
1	1	0	1	1	1	1		
1	1	1	0	1	1	0		

Step 3 concluded

- Using the characteristic equations:

$$Q_1(t+1) = K_1'Q_1(t) + J_1Q_1'(t)$$

$$Q_0(t+1) = K_0'Q_0(t) + J_0Q_0'(t)$$

Or the characteristic table

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

Present State		Inputs X	FF Inputs				Next State	
Q ₁	Q ₀		J ₁	K ₁	J ₀	K ₀	Q ₁	Q ₀
0	0	0	0	0	0	1	0	
0	0	1	0	1	1	0		
0	1	0	1	1	0	1		
0	1	1	0	1	1	0		
1	0	0	0	0	1	1		
1	0	1	0	1	1	0		
1	1	0	1	1	1	1	0	
1	1	1	0	1	1	0		

Step 3 concluded

- Finally, here are the next states for Q_1 and Q_0 , using these equations:

$$Q_1(t+1) = K_1'Q_1(t) + J_1Q_1'(t)$$

$$Q_0(t+1) = K_0'Q_0(t) + J_0Q_0'(t)$$

Present State		Inputs X	FF Inputs				Next State	
Q_1	Q_0		J_1	K_1	J_0	K_0	Q_1	Q_0
0	0	0	0	0	0	1	0	0
0	0	1	0	1	1	0	0	1
0	1	0	1	1	0	1	1	0
0	1	1	0	1	1	0	0	1
1	0	0	0	0	1	1	1	1
1	0	1	0	1	1	0	0	1
1	1	0	1	1	1	1	0	0
1	1	1	0	1	1	0	0	1

Getting the state table columns straight

- The table starts with **Present State** and **Inputs**
 - **Present State** and **Inputs** yield **FF Inputs**
 - **Present State** and **FF Inputs** yield **Next State**, based on the flip-flop characteristic tables
 - **Present State** and **Inputs** yield **Output**

Present State		Inputs	FF Inputs				Next State		Outputs
Q ₁	Q ₀		J ₁	K ₁	J ₀	K ₀	Q ₁	Q ₀	
0	0	0	0	0	0	1	0	0	0
0	0	1	0	1	1	0	0	1	0
0	1	0	1	1	0	1	1	0	0
0	1	1	0	1	1	0	0	1	0
1	0	0	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0	1	0
1	1	0	1	1	1	1	0	0	0
1	1	1	0	1	1	0	0	1	1

A different look


Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

Present State		Next State				Output Z	
		Input $X=0$		Input $X=1$		$X=0$	$X=1$
Q_1	Q_0						
0	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	1

State diagrams (Mealy model)


- We can also represent the state table graphically with a state diagram
- A diagram corresponding to our example state table is shown below

Present State		Inputs X	Next State		Outputs Z
Q ₁	Q ₀		Q ₁	Q ₀	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

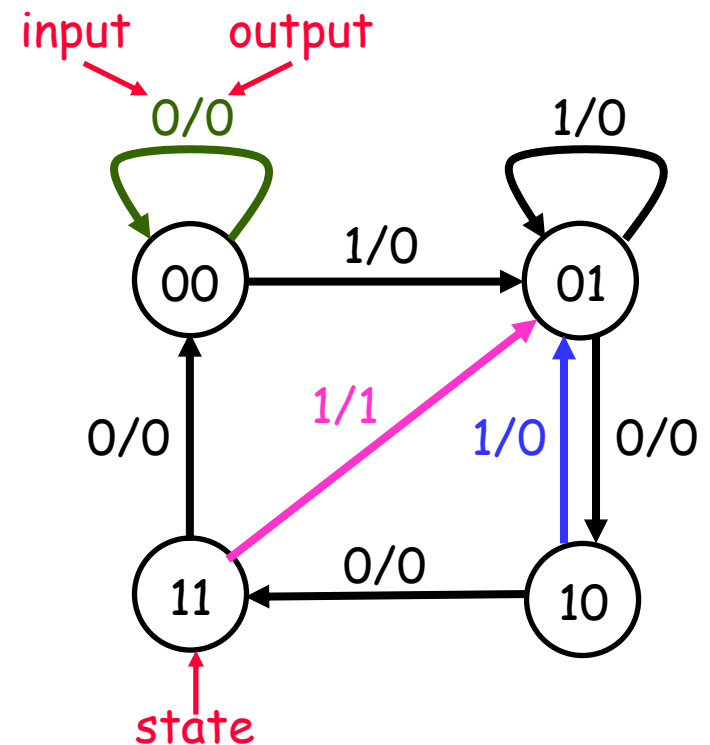


Sizes of state diagrams

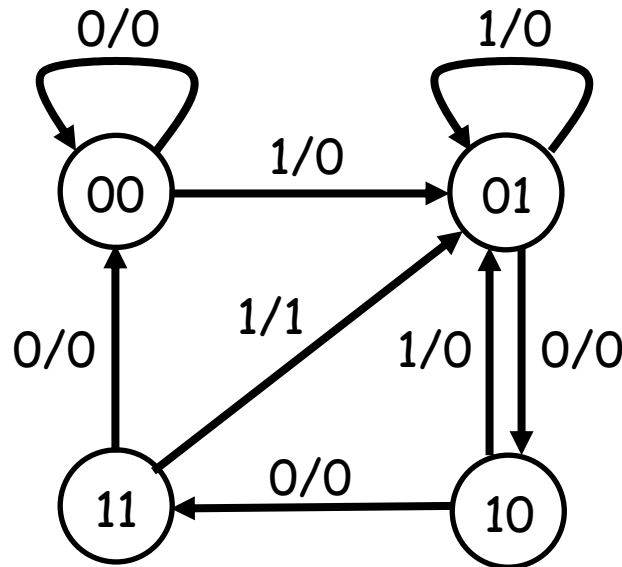- Always check the size of your state diagrams
 - If there are n flip-flops, there should be 2^n nodes in the diagram
 - If there are m inputs, then each node will have 2^m outgoing arrows
- In our example,
 - We have two flip-flops, and thus four states or nodes.
 - There is one input, so each node has two outgoing arrows.




Moore type circuit

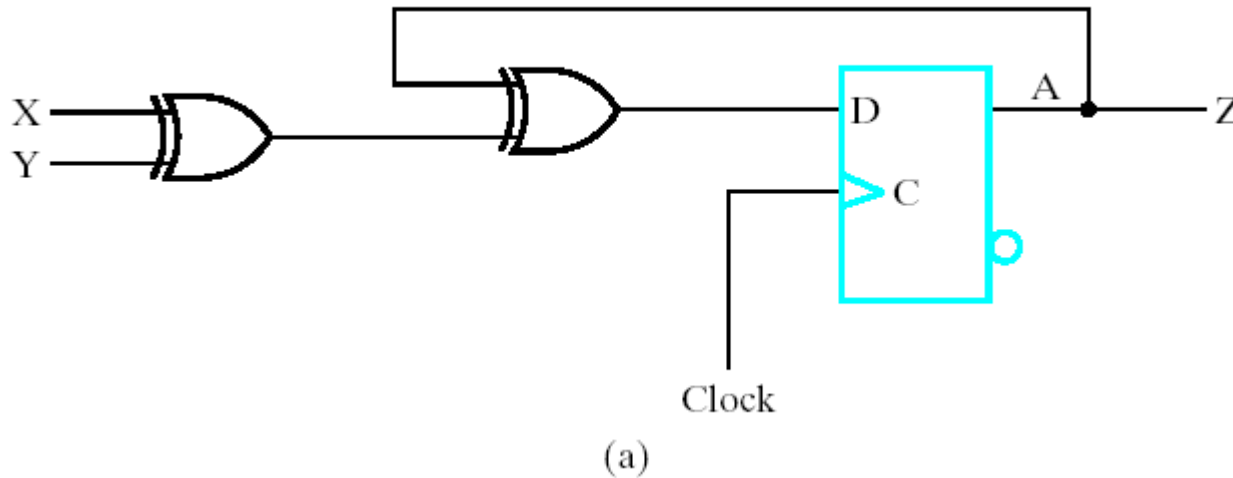

- Two inputs: X and Y; One output: Z
- One state: A
- Note that $Z = A$, just a function of the current state

State table (Moore)

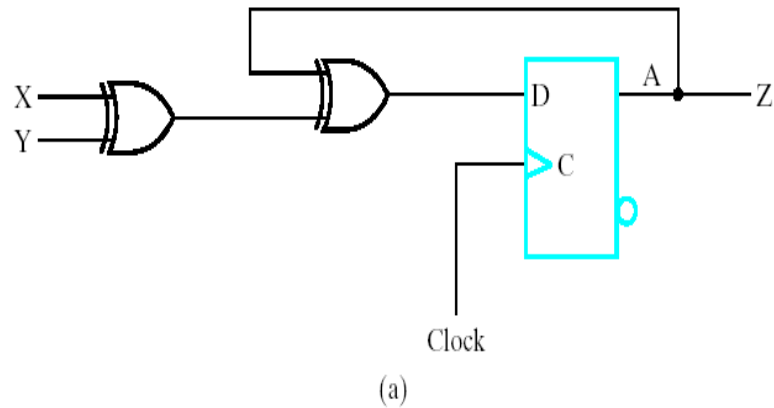

Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


(b) State table

Present State A	Next State				Output Z
	Inputs XY				
	00	01	10	11	
0	0	1	1	0	0
1	1	0	0	1	1

State diagram (Moore)

Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(b) State table

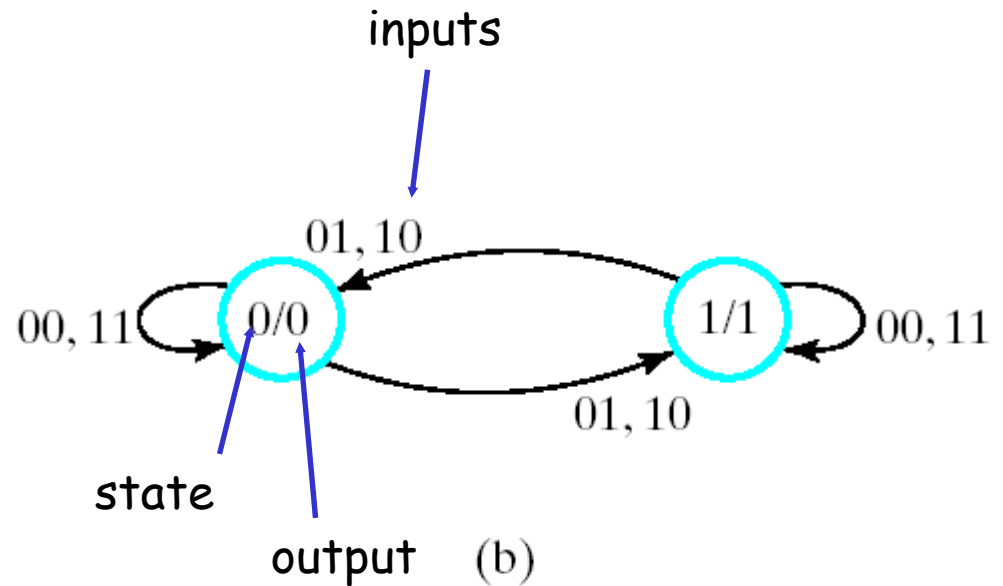

Sequential circuit analysis summary

- To analyze sequential circuits, you have to:
 - Find Boolean expressions for the outputs of the circuit and the flip-flop inputs
 - Use these expressions to fill in the output and flip-flop input columns in the state table
 - Finally, use the characteristic equation or characteristic table of the flip-flop to fill in the next state columns.
- The result of sequential circuit analysis is a state table or a state diagram describing the circuit

