

# **CSE1003**

## **Digital Logic and Design**

### **Module 2**

### **BOOLEAN ALGEBRA L2**

**Dr. S. Hemamalini**  
**Professor**  
**School of Electrical Engineering**  
**VIT Chennai**

## **Module 2**

# **BOOLEAN ALGEBRA**

**8 hrs**

### Boolean algebra

- Properties of Boolean algebra
- Boolean functions
- Canonical and Standard forms
- Logic gates - Universal gates
- Karnaugh map - Don't care conditions
- Tabulation Method

## Boolean Algebra

Logic 0	Logic 1
False	True
Off	On
Low	High
No	Yes
Open switch	Closed switch

1854  
George Boole

- Boolean algebra is mathematics of logic.
- The algebra which deals with the logical operations of binary variables is called Boolean Algebra.
- **Boolean algebra** is a means for expressing the relationship between a logic circuit's inputs and outputs.
- The inputs are considered **logic variables** whose logic levels at any time determine the output levels.
- It is one of the most basic tools available to the logic designer and thus can be effectively used for simplification of complex logic expressions.

# Boolean algebra

## Boolean function

- Is an **expression** formed with binary variables, Boolean operators and the equality sign.
- Can also be represented in the form of a truth table.

**Expression:** a set of literals (possibly with repeats) combined with logic operations (and possibly ordered by parentheses)

$$A B + C \quad (\bar{A} + B) C$$

**Equation:** expression1 = expression2

$$(\bar{A} + B) C = ((\bar{A}) + B) C$$

**Function of (possibly several) variables:** an equation where the left hand side is defined by the right hand side

$$f(A, B, C) = ((\bar{A}) + B) C$$

# Boolean algebra

## *Variables, Literals and Terms in Boolean Expressions*

$$\begin{array}{r} 25 \quad 1 \\ 72 \quad \quad \\ \hline 0.8 \quad 2 \quad 0 \\ 0 \quad \quad \end{array}$$

- **Variables** are the letters in a Boolean expression which represents a physical quantity such as a voltage signal. They may take on the value '0' or '1'.
- The complement of a variable is not considered as a separate variable. Each occurrence of a variable or its complement is called a **literal**.
- A **term** is the expression formed by literals and operations at one level.

$$\begin{aligned} &\overline{A} + A.B + A.\overline{C} + \overline{A}.B.C \\ &(\overline{P} + Q).(R + \overline{S}).(P + \overline{Q} + R) \end{aligned}$$


$$\begin{array}{ccc} A & B & C \\ \overline{A} & \overline{B} & \overline{C} \end{array}$$

# BOOLEAN THEOREMS


- help to simplify logic expressions and logic circuits

## Single-variable theorems


AND

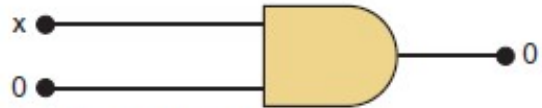


(1)  $x \cdot 0 = 0$

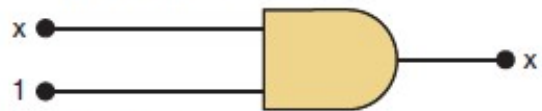

(2)  $x \cdot 1 = x$

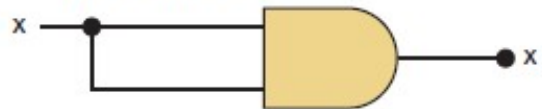


(3)  $x \cdot x = x$

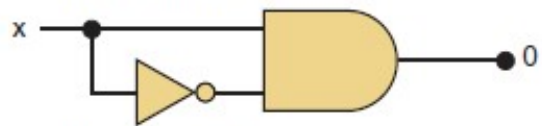


(4)  $x \cdot \bar{x} = 0$


OR

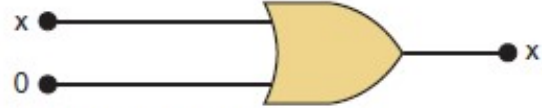


(5)  $x + 0 = x$

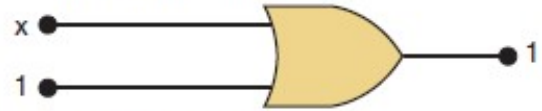

(6)  $x + 1 = 1$

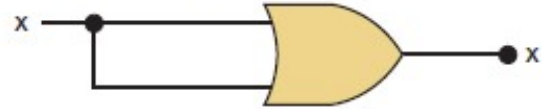

(7)  $x + x = x$

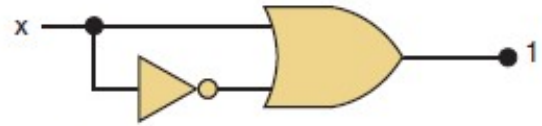


(8)  $x + \bar{x} = 1$

## Laws of Boolean Algebra


### ◆ Commutative Laws

$$A + B = B + A$$

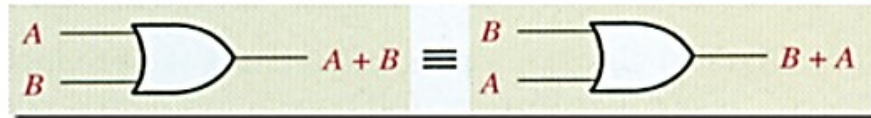


$$A \cdot B = B \cdot A$$

$$AB = BA$$

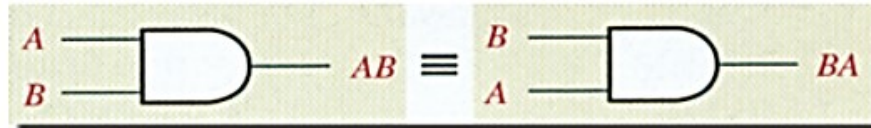


### ◆ Associative Laws

$$A + (B + C) = (A + B) + C$$

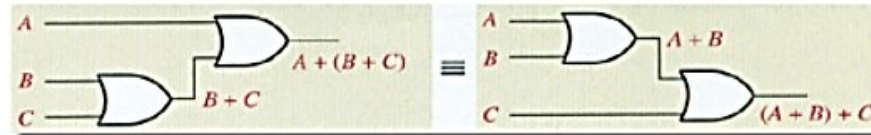

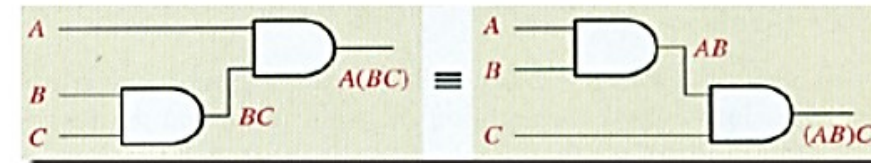
$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$



### ◆ Distributive Law

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$A(B + C) = AB + AC$$


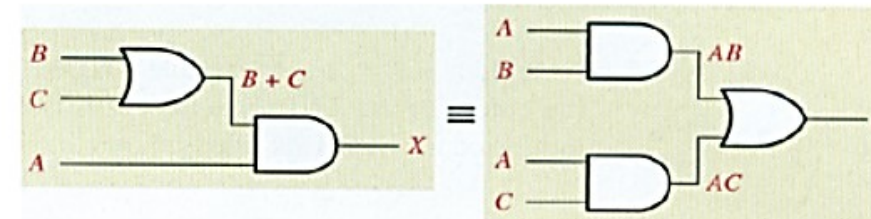


# DeMorgan's Theorem

**DeMorgan's theorems** are extremely useful in simplifying expressions in which a product or sum of variables is inverted.

The complement of a product of variables is equal to the sum of the complements of the variables

$$\overline{XY} = \bar{X} + \bar{Y}$$

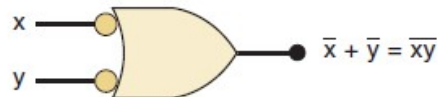
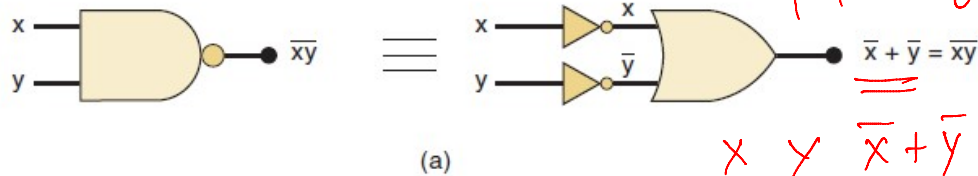


-ve OR (b)

X	Y	$\overline{XY}$
0	0	1
0	1	1
1	0	1
1	1	0

The complement of a sum of variables is equal to the product of the complements of the variables.
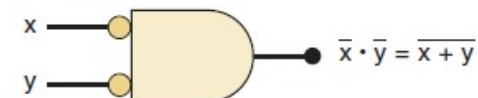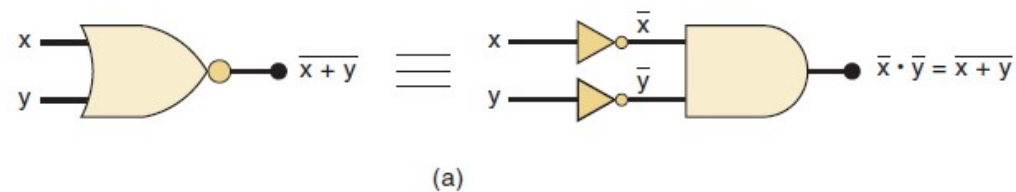
$$\overline{X + Y} = \bar{X} \cdot \bar{Y}$$




-ve AND (b)



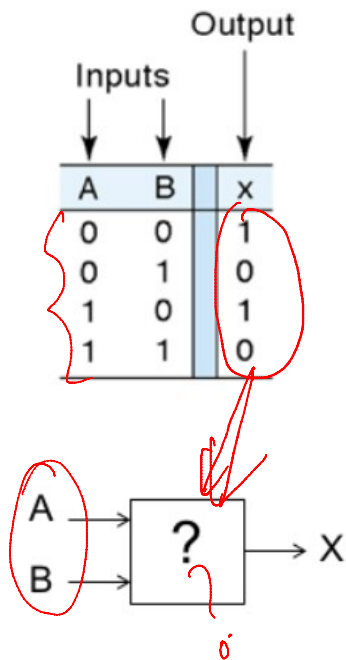
# Boolean Logic

- Truth Table: all combinations of input variables
- k variables  $\rightarrow 2^k$  input combinations


Truth Tables specifies how a logic circuit's output depends on the logic levels present at the inputs.



A	B	C	x
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

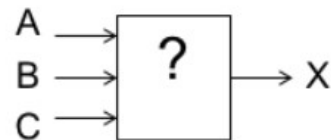

A	B	C	D	x
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

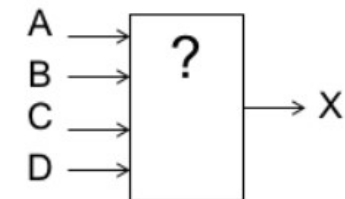

## Laws of Boolean Algebra used for simplifying logical expressions

$(A^l = \bar{A})$  denotes the complement/inverse/NOT of  $A$ )

$$A + 0 = A$$

$$A + 1 = 1$$

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A + A = A$$

$$A + A^l = 1$$

$$A \cdot A = A$$

$$A \cdot A^l = 0$$

$$(A^l)^l = A$$

$$A + AB = A$$

$$A + A^l B = A + B$$

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$(A + B)(A + C) = A + BC$$


$$A \cdot B \cdot 1 = A \cdot B$$

$$A + B + 1 = 1$$


$$A \cdot B \cdot 0 = 0$$

$$A + B + 0 = A + B$$



## UNIVERSALITY OF NAND GATES

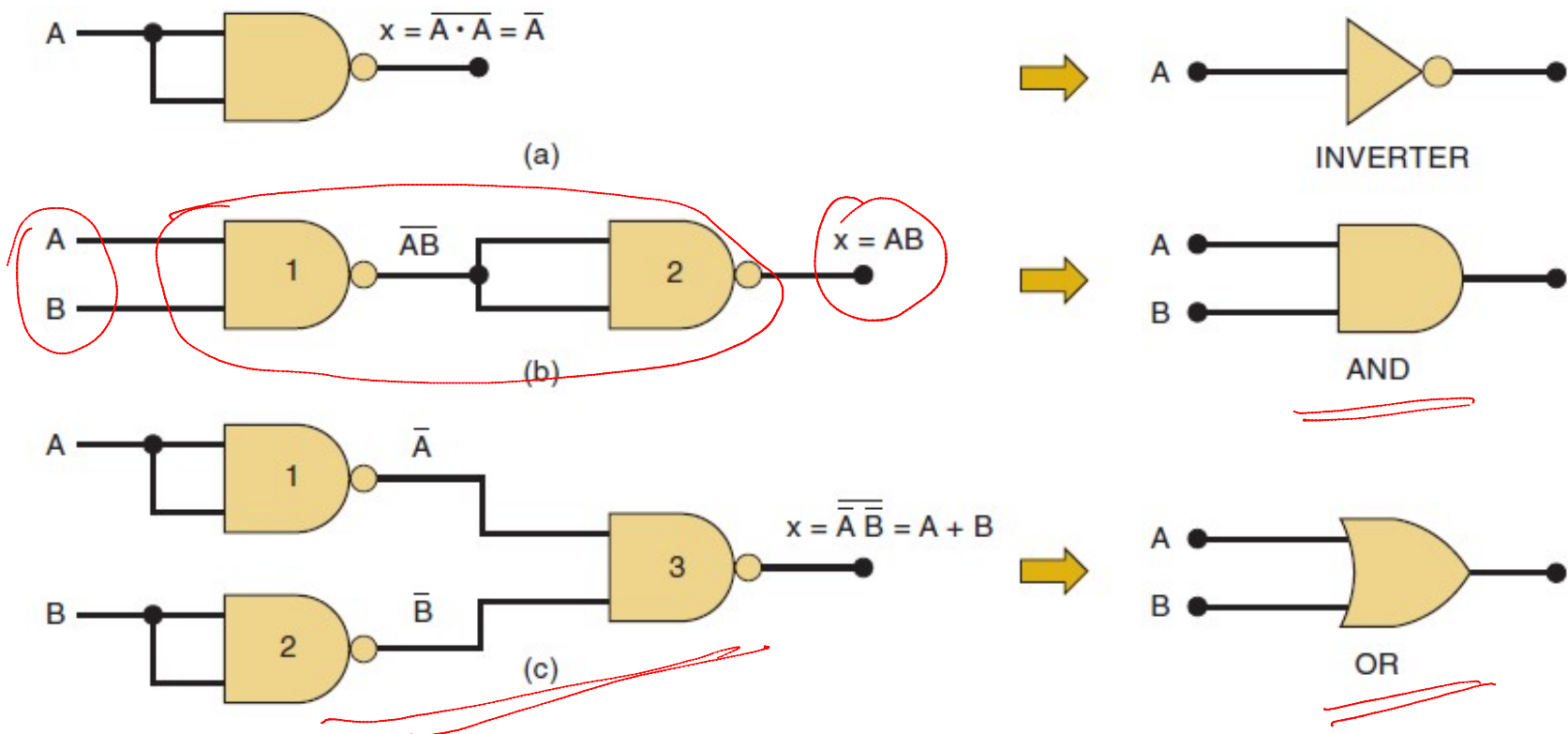



## UNIVERSALITY OF NOR GATES

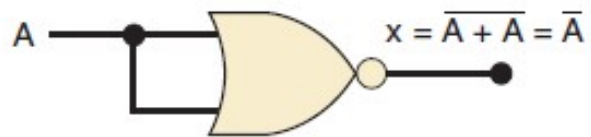


(a)

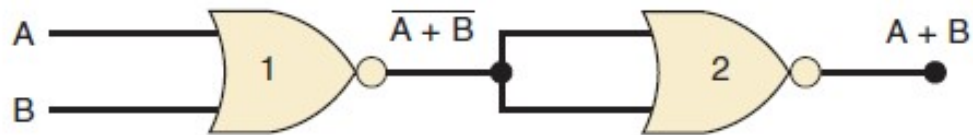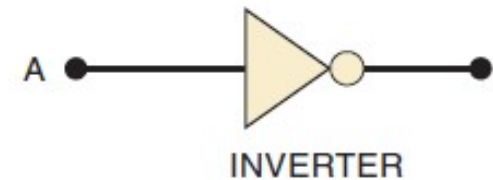

(b)

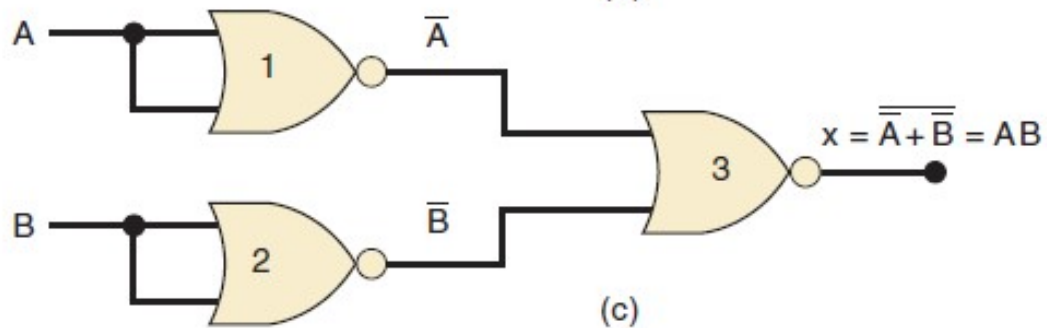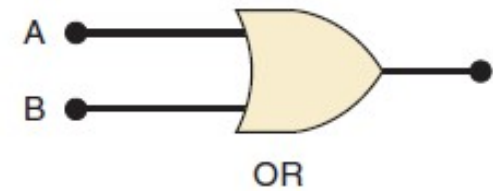

(c)

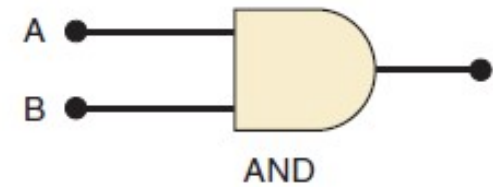

## Precedence rules in Boolean algebra


- Scan the expression from left to right.
- First evaluate expression enclosed in parentheses. ✓
- Perform all the complement operations.
- Perform all the AND operations in the order.
- Perform all the OR operations.

## DESCRIBING LOGIC CIRCUITS ALGEBRAICALLY FROM BOOLEAN EXPRESSIONS

A Boolean function from an algebraic expression can be realized to a logic diagram composed of logic gates.


$$x = A \cdot B + C$$

2 gates  
1 AND  
1 OR

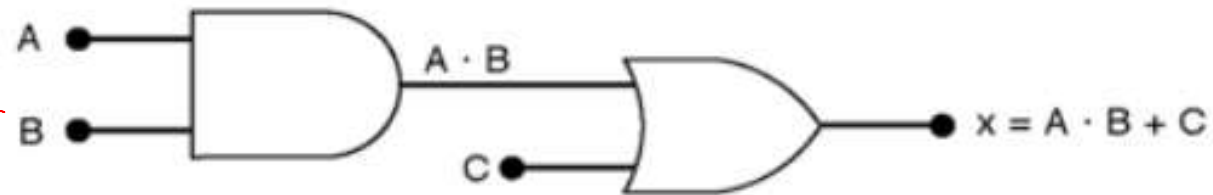

$$y = AC + B\bar{C} + \bar{A}BC$$


Total 4  
AND: 3  
OR: 2  
NOT: 2

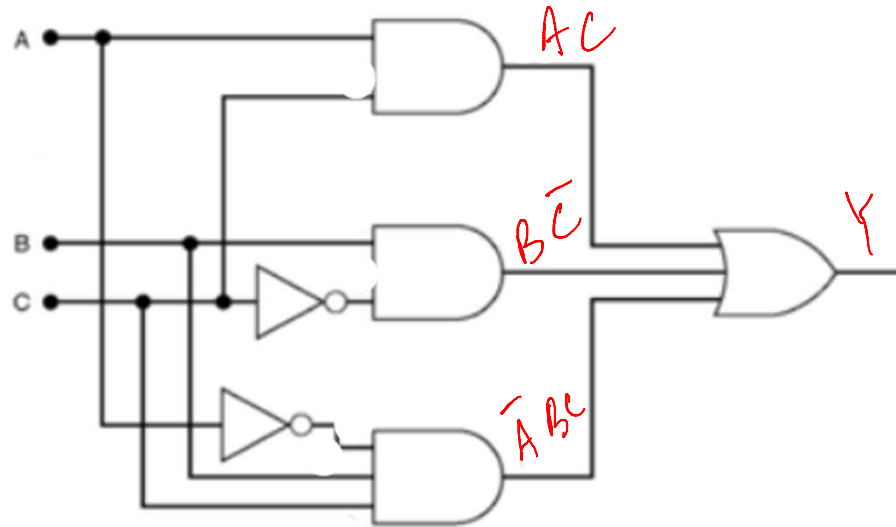



$$y = AC + B\bar{C} + \bar{A}BC$$

## DESCRIBING LOGIC CIRCUITS ALGEBRAICALLY FROM BOOLEAN EXPRESSIONS

$$x = (A + B)(\bar{B} + C)$$

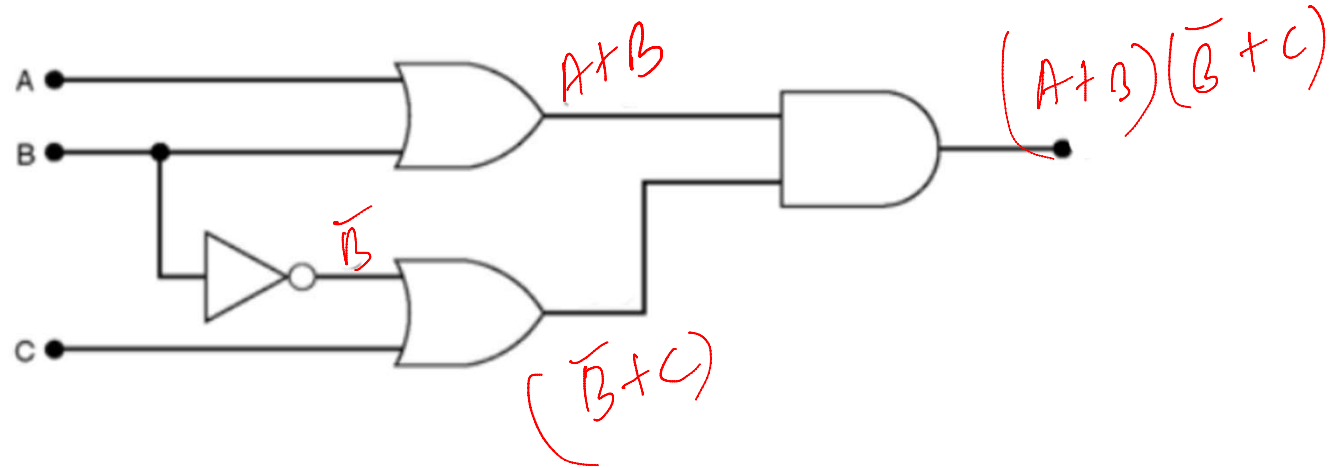
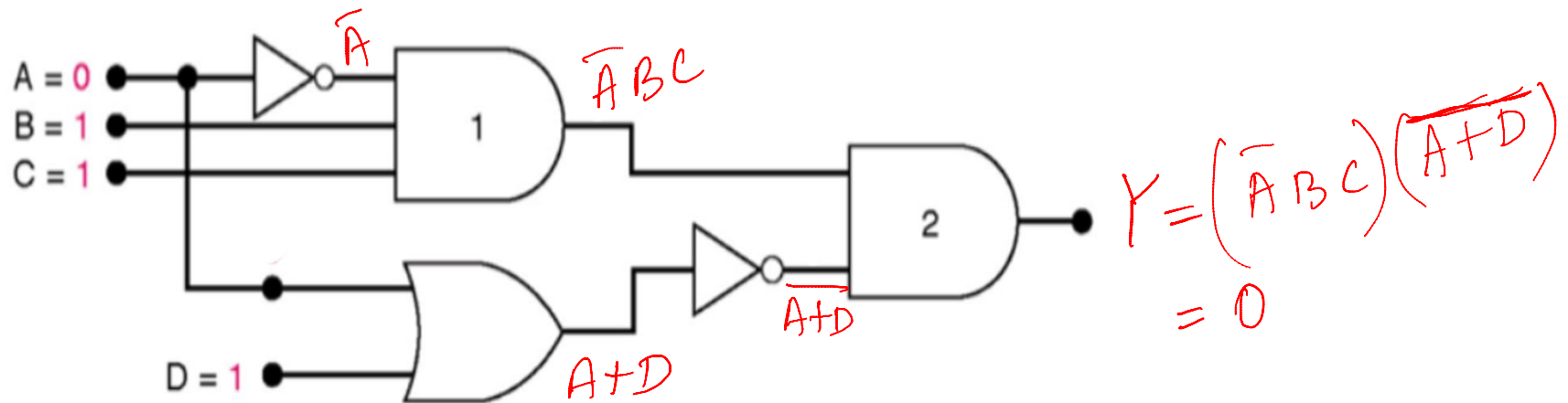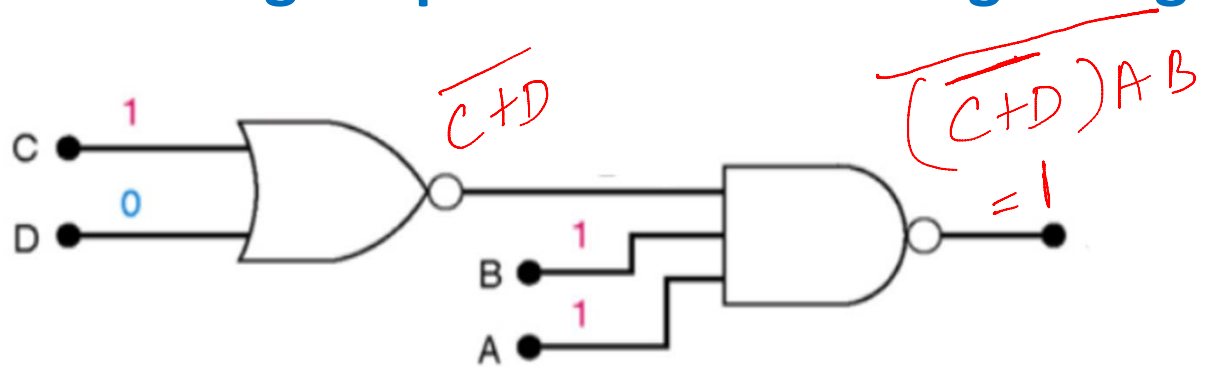
## Determining output value from a logic diagram





## Simplification Techniques

- The primary objective of all simplification procedures is to obtain an expression that has the minimum number of terms.
- Obtaining an expression with the minimum number of literals is usually the secondary objective.
- If there is more than one possible solution with the same number of terms, the one having the minimum number of literals is the choice.

Algebraic Method  
K-Map "  
Tabulation

$$\underline{\underline{A + C}}$$

$$Y = \cancel{ABC} + \cancel{\overline{A}B\overline{C}} + \cancel{A\overline{C}} + \cancel{\overline{B}CA}$$

4 terms

## Simplify using Boolean Algebra

$$y = A\bar{B}D + A\bar{B}\bar{D}$$



$$y = A\bar{B}$$

$$A\bar{B}(D + \bar{D}) = A\bar{B} \quad D + \bar{D} = 1$$

$$z = (\bar{A} + B)(A + B)$$



$$z = B$$

$$\begin{aligned} \bar{A}A + AB + \bar{A}B + BB \\ = 0 + AB + \bar{A}B + B \\ = 0 + (A + \bar{A})B + B \\ = B + B = B \end{aligned}$$

$$x = ACD + \bar{A}BCD$$



$$x = ACD + BCD$$

$$(A + \bar{A}B)CD = (A + B)CD = ACD + BCD$$

$$z = (\bar{A} + C)(B + \bar{D})$$




$$z = A\bar{C} + \bar{B}D$$

$$\begin{aligned} (\bar{A} + C) + (B + \bar{D}) &= \bar{A} \cdot \bar{C} + \bar{B} \cdot \bar{D} \\ &= A\bar{C} + \bar{B}D \end{aligned}$$
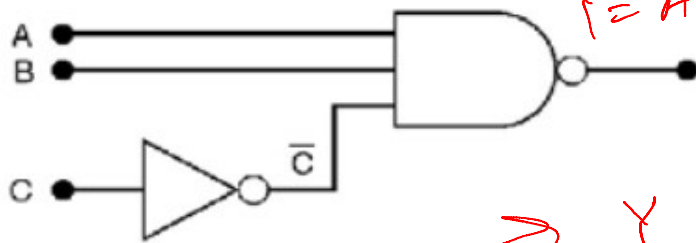
## Simplify using Boolean Algebra

Determine the output expression for the circuit below and simplify it using DeMorgan's Theorem



$$Y = A \cdot B \cdot \bar{C}$$


$$Y = \bar{A} + \bar{B} + C$$

2 NOT  
1 OR.

$$z = \overline{A \cdot B \cdot \bar{C}} = \bar{A} + \bar{B} + \bar{\bar{C}} = \bar{A} + \bar{B} + C$$

Simplify the logic circuit shown in Figure

*Given circuit*

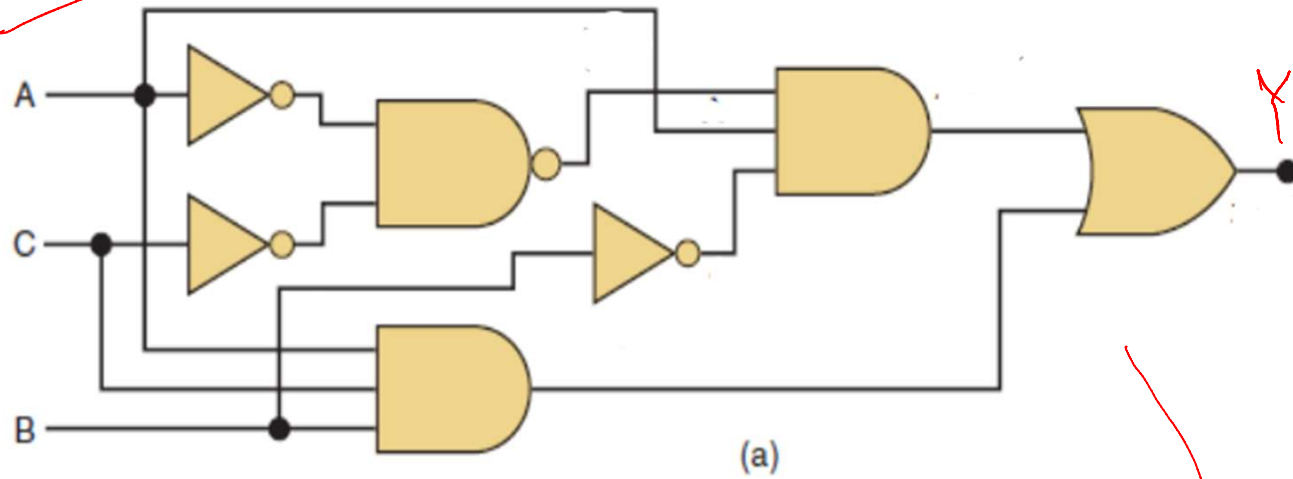

$X = ?$

*↓ simplify.*

*simplified ckt.*

