

# **CSE1003-Digital Logic Design**

## **Module:5 Sequential Circuits-I Part-2**

**Dr.Penchalaiah Palla**

Dept. of Micro and Nanoelectronics  
School of Electronics Engineering,VIT,  
Vellore

# Module:5 Sequential Circuits-I

<b>Module:5</b>	<b>SEQUENTIAL CIRCUITS – I</b>	<b>6 hours</b>
-----------------	--------------------------------	----------------

Flip Flops - Sequential Circuit: Design and Analysis - Finite State Machine: Moore and Mealy model - Sequence Detector.

<b>Module:6</b>	<b>SEQUENTIAL CIRCUITS – II</b>	<b>7 hours</b>
-----------------	---------------------------------	----------------

Registers - Shift Registers - Counters - Ripple and Synchronous Counters - Modulo counters - Ring and Johnson counters

# Introduction: Sequential Circuits

## ◆ Combinational

- The outputs depend only on the current input values
- It uses only logic gates

## ◆ Sequential

- The outputs depend on the current and past input values
- It uses logic gates and storage elements
- Example
  - ✓ Vending machine
- They are referred as finite state machines since they have a finite number of states

# Sequential Logic Design with Flip-flops

- Introduction
- Flip-flop Characteristic Tables
- Sequential Circuit Analysis
- Flip-flop Input Functions
- Analysis: Example #2
- Analysis: Example #3
- Flip-flop Excitation Tables



# Sequential Logic Design with Flip-flops

- Sequential Circuit Design
- Design: Example #1
- Design: Example #2
- Design: Example #3
- Design of Synchronous Counters



# Introduction

- Sequential circuits has an extra dimension – *time*.
- Combinational circuit output depends only on the present inputs
- Sequential circuit output depends on the history of past inputs as well
- More powerful than combinational circuit, able to model situations that cannot be modeled by combinational circuits
- Building blocks of **synchronous sequential logic** circuits: *gates* and *flip-flops*.
- Flip-flops make up the *memory*  $M$  while the gates form one or more combinational subcircuits  $C_1, C_2, \dots, C_q$ .



# Difference Between Analysis and Design

- *Analysis*: Starting from a circuit diagram, derive the state table or state diagram.
- *Characteristic tables* are used in analysis.
- *Design*: Starting from a set of specifications (in the form of state equations, state table, or state diagram), derive the logic circuit.
- *Excitation tables* are used in design.

# Flip-flop Characteristic Tables

- Each type of flip-flop has its own behavior. The **characteristic tables** for the various types of flip-flops are shown below:

$J$	$K$	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q(t)'$	Toggle

JK Flip-flop

$S$	$R$	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Unpredictable

SR Flip-flop

$D$	$Q(t+1)$
0	0      Reset
1	1      Set

D Flip-flop

$T$	$Q(t+1)$
0	$Q(t)$ No change
1	$Q(t)'$ Toggle

T Flip-flop





# Sequential Circuit Analysis

- Given a sequential circuit diagram, analyze its behaviour by deriving its *state table* and hence its *state diagram*.
- Requires *state equations* to be derived for the flip-flop inputs, as well as *output functions* for the circuit outputs other than the flip-flops (if any).
- We use  $A(t)$  and  $A(t+1)$  to represent the present state and next state, respectively, of a flip-flop represented by  $A$ .
- Alternatively, we could simply use  $A$  and  $A^+$  for the present state and next state respectively.



# Sequential Circuit Analysis

- Example #1 (using D flip-flops):

State equations:

$$A^+ = A.x + B.x$$

$$B^+ = A'.x$$

Output function:

$$y = (A + B).x'$$

 


Figure 1.



# Sequential Circuit Analysis

- From the *state equations* and *output function*, we derive the *state table*, consisting of all possible binary combinations of present states and inputs.
- State table
  - ❖ Similar to truth table.
  - ❖ Inputs and present state on the left side.
  - ❖ Outputs and next state on the right side.
- $m$  flip-flops and  $n$  inputs  $\rightarrow 2^{m+n}$  rows.



# Sequential Circuit Analysis

- State table for the circuit of Figure 1:

State equations:

$$A^+ = A.x + B.x$$

$$B^+ = A'.x$$

Output function:

$$y = (A + B).x'$$

Present State		Input	Next State		Output
A	B		A <sup>+</sup>	B <sup>+</sup>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0



# Sequential Circuit Analysis

- Alternate form of state table:

Present State		Input	Next State		Output
A	B		A <sup>+</sup>	B <sup>+</sup>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
AB	A <sup>+</sup> B <sup>+</sup>	A <sup>+</sup> B <sup>+</sup>	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0



# Sequential Circuit Analysis



- From the *state table*, we can draw the *state diagram*.
- State diagram
  - ❖ Each state is denoted by a circle.
  - ❖ Each arrow (between two circles) denotes a transition of the sequential circuit (a row in state table).
  - ❖ A label of the form  $a/b$  is attached to each arrow where  $a$  denotes the inputs while  $b$  denotes the outputs of the circuit in that transition.
- Each combination of the flip-flop values represents a state. Hence,  $m$  flip-flops  $\rightarrow$  up to  $2^m$  states.



# Sequential Circuit Analysis

- State diagram of the circuit of Figure 1:

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
AB	$A^+B^+$	$A^+B^+$	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

  

# Flip-flop Input Functions

- The outputs of a sequential circuit are functions of the present states of the flip-flops and the inputs. These are described algebraically by the *circuit output functions*.
  - ❖ In Figure 1:  $y = (A + B).x'$
- The part of the circuit that generates inputs to the flip-flops are described algebraically by the *flip-flop input functions* (or *flip-flop input equations*).
- The flip-flop input functions determine the next state generation.
- From the flip-flop input functions and the characteristic tables of the flip-flops, we obtain the next states of the flip-flops.






# Flip-flop Input Functions

- Example: circuit with a JK flip-flop.
- We use 2 letters to denote each flip-flop input: the first letter denotes the input of the flip-flop ( $J$  or  $K$  for JK flip-flop,  $S$  or  $R$  for SR flip-flop,  $D$  for D flip-flop,  $T$  for T flip-flop) and the second letter denotes the name of the flip-flop.

$$JA = B.C'.x + B'.C.x'$$

$$KA = B + y$$

 

# Flip-flop Input Functions

- In Figure 1, we obtain the following state equations by observing that  $Q^+ = DQ$  for a D flip-flop:

$$A^+ = A.x + B.x \quad (\text{since } DA = A.x + B.x)$$

$$B^+ = A'.x \quad (\text{since } DB = A'.x)$$

 


Figure 1.

- [illegible]

Figure 2.

- $$KB = A'.x + A.x' = A \oplus x$$

# Analysis: Example #2

- Flip-flop input functions:

$$JA = B$$

$$JB = x'$$

$$KA = B.x'$$

$$KB = A'.x + A.x' = A \oplus x$$

- Fill the state table using the above functions, knowing the characteristics of the flip-flops used.

<i>J</i>	<i>K</i>	<i>Q(t+1)</i>	Comments
0	0	<i>Q(t)</i>	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q(t)'</i>	Toggle



Present state		Input <i>x</i>	Next state		Flip-flop inputs			
<i>A</i>	<i>B</i>		<i>A</i> <sup>+</sup>	<i>B</i> <sup>+</sup>	<i>JA</i>	<i>KA</i>	<i>JB</i>	<i>KB</i>
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0



# Analysis: Example #2

- Draw the state diagram from the state table.

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

  

# Analysis: Example #3

- Derive the state table and state diagram of the following circuit.

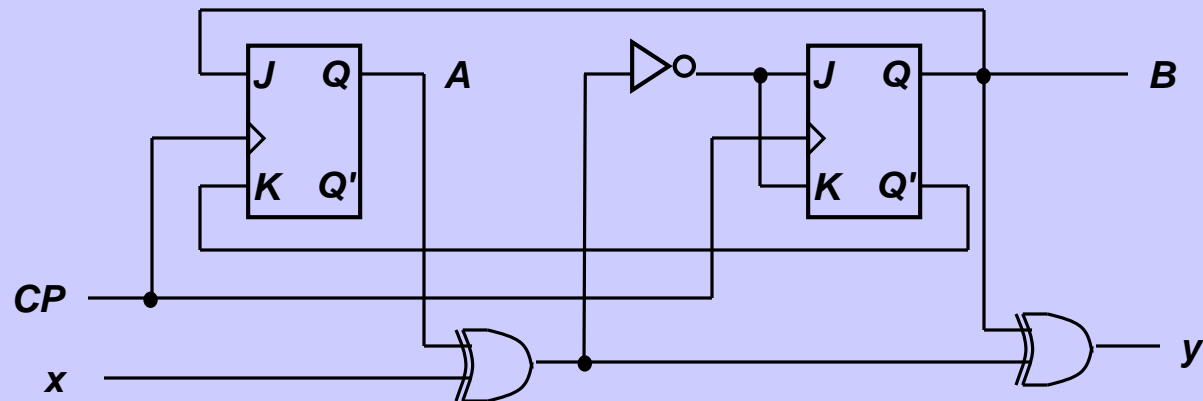


Figure 3.

- Flip-flop input functions:

$$JA = B$$

$$JB = KB = (A \oplus x)' = A.x + A'.x'$$

$$KA = B'$$

# Analysis: Example #3

- Flip-flop input functions:

$$JA = B$$

$$JB = KB = (A \oplus x)' = A.x + A'.x'$$

$$KA = B'$$

- State table:


Present state		Input <u>x</u>	Next state		Output <u>y</u>	Flip-flop inputs			
<u>A</u>	<u>B</u>		<u>A<sup>+</sup></u>	<u>B<sup>+</sup></u>		<u>JA</u>	<u>KA</u>	<u>JB</u>	<u>KB</u>
0	0	0	0	1	0	0	1	1	1
0	0	1	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	1	1
0	1	1	1	1	0	1	0	0	0
1	0	0	0	0	1	0	1	0	0
1	0	1	0	1	0	0	1	1	1
1	1	0	1	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1	1



# Analysis: Example #3

- State diagram:

Present state		Input $x$	Next state		Output $y$	Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$		$JA$	$KA$	$JB$	$KB$
0	0	0	0	1	0	0	1	1	1
0	0	1	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	1	1
0	1	1	1	1	0	1	0	0	0
1	0	0	0	0	1	0	1	0	0
1	0	1	0	1	0	0	1	1	1
1	1	0	1	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1	1

 



# Flip-flop Excitation Tables

- *Design*: Starting from a set of specifications (in the form of state equations, state table, or state diagram), derive the logic circuit.
- *Excitation tables* are used in design.



# Flip-flop Excitation Tables

- *Excitation tables*: given the required transition from present state to next state, determine the flip-flop input(s).

$Q$	$Q^+$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-flop

$Q$	$Q^+$	$S$	$R$
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

SR Flip-flop

$Q$	$Q^+$	$D$
0	0	0
0	1	1
1	0	0
1	1	1

D Flip-flop

$Q$	$Q^+$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

T Flip-flop



# Sequential Circuit Design


## ■ Design procedure:

- ❖ Start with circuit specifications – description of circuit behaviour.
- ❖ Derive the state table.
- ❖ Perform state reduction if necessary.
- ❖ Perform state assignment.
- ❖ Determine number of flip-flops and label them.
- ❖ Choose the type of flip-flop to be used.
- ❖ Derive circuit excitation and output tables from the state table.
- ❖ Derive circuit output functions and flip-flop input functions.
- ❖ Draw the logic diagram.



 
# Design: Example #1

- Given the following state diagram, design the sequential circuit using JK flip-flops.


 
# Design: Example #1

- Circuit state/excitation table, using JK flip-flops.



Present State	Next State	
	$x=0$	$x=1$
$AB$	$A^+B^+$	$A^+B^+$
00	00	01
01	10	01
10	10	11
11	11	00


$Q$	$Q^+$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-flop's excitation table.

Present state		Input	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

# Design: Example #1





- Block diagram.

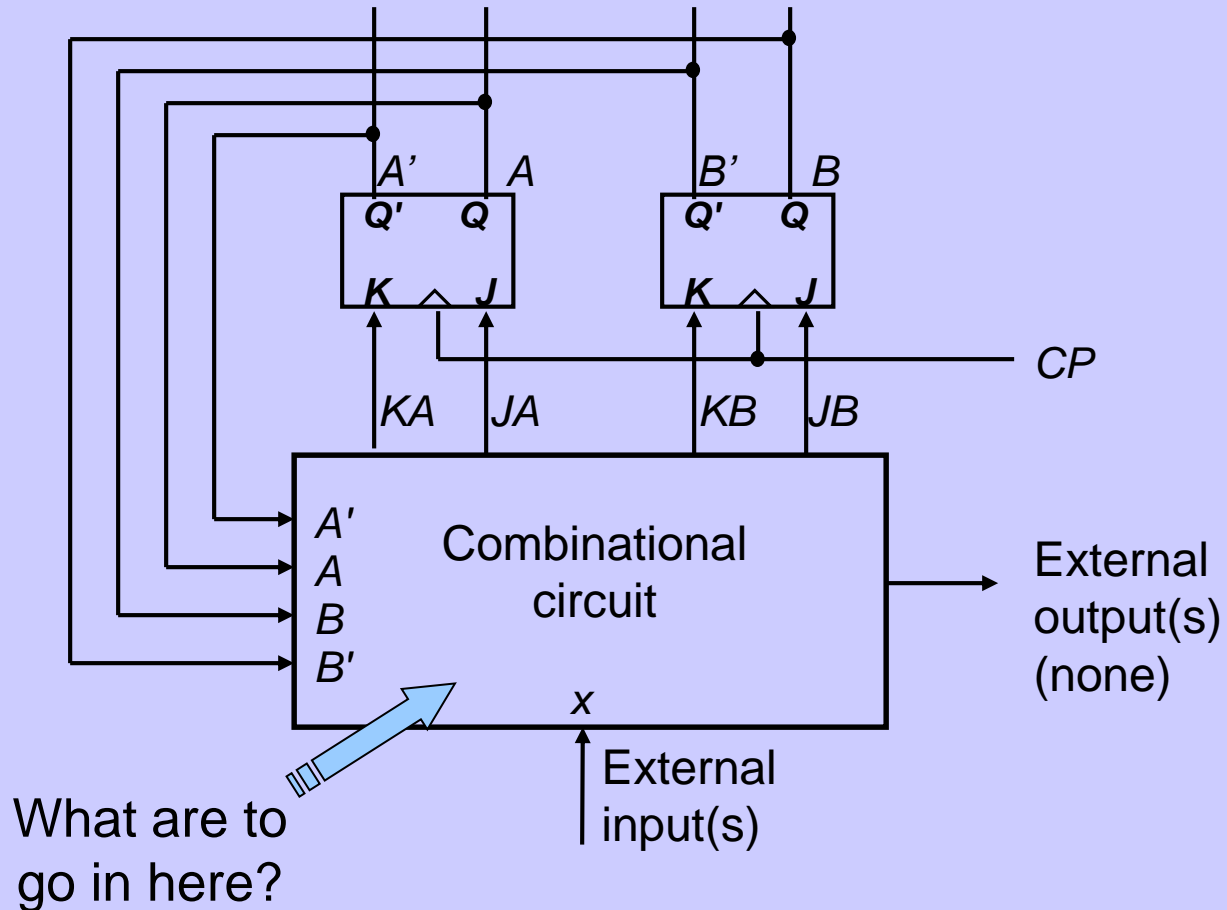

# Design: Example #1

- From state table, get flip-flop input functions.

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

    

- Logic diagram:

$$KA = B.x$$

$$KB = (A \oplus x)'$$





# Design: Example #2

- Design, using D flip-flops, the circuit based on the state table below. (Exercise: Design it using JK flip-flops.)

Present state		Input	Next state		Output
A	B		A <sup>+</sup>	B <sup>+</sup>	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0



# Design: Example #2

- Determine expressions for flip-flop inputs and the circuit output  $y$ .

Present state		Input $x$	Next state		Output $y$
$A$	$B$		$A^+$	$B^+$	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

$$DA(A, B, x) = \Sigma m(2,4,5,6)$$

$$DB(A, B, x) = \Sigma m(1,3,5,6)$$

$$y(A, B, x) = \Sigma m(1,5)$$

		$Bx$			
		00	01	11	10
$A$	0				1
	1	1	1		1

$$DA = A.B' + B.x'$$

		$Bx$			
		00	01	11	10
$A$	0		1	1	
	1		1		1

$$DB = A'.x + B'.x + A.B.x'$$

		$Bx$			
		00	01	11	10
$A$	0		1		
	1		1		

$$y = B'.x$$


# Design: Example #2

- From derived expressions, draw logic diagram:

$$DA = A.B' + B.x'$$

$$DB = A'.x + B'.x + A.B.x'$$

$$y = B'.x$$

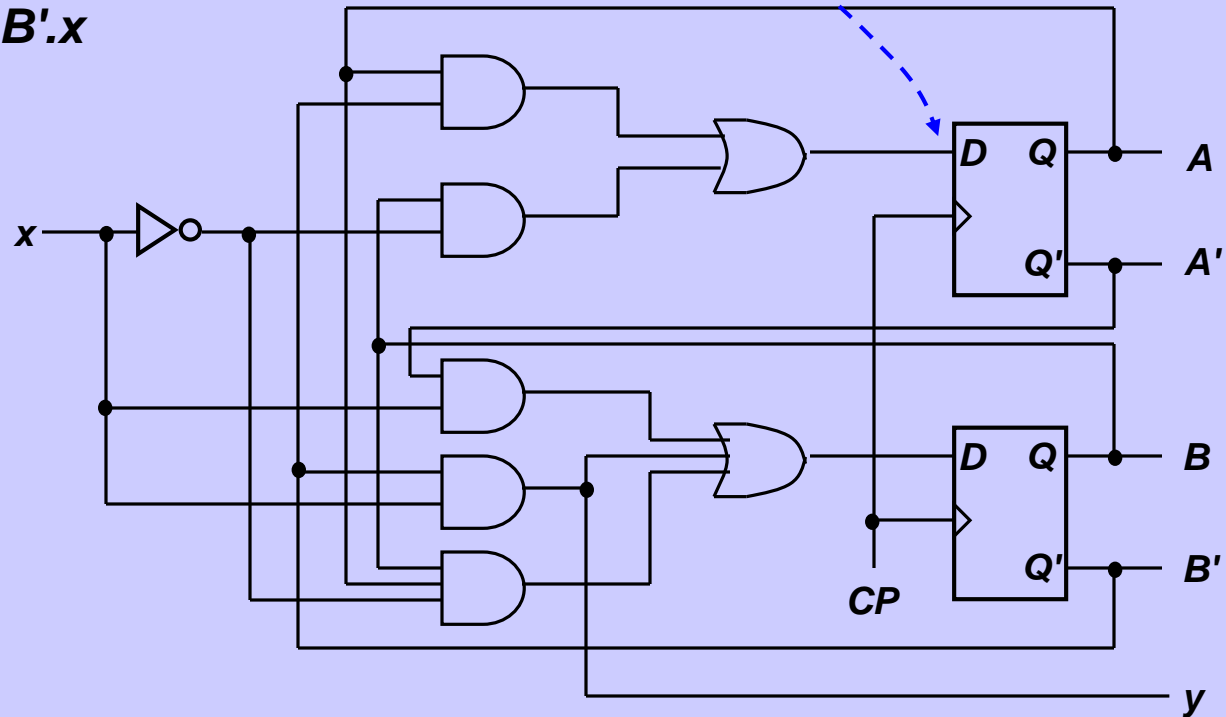

# Design: Example #3

- Design with unused states.

Present state			Input	Next state			Flip-flop inputs						Output
A	B	C		A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	SA	RA	SB	RB	SC	RC	y
0	0	1	0	0	0	1	0	X	0	X	X	0	0
0	0	1	1	0	1	0	0	X	1	0	0	1	0
0	1	0	0	0	1	1	0	X	X	0	1	0	0
0	1	0	1	1	0	0	1	0	0	1	0	X	0
0	1	1	0	0	0	1	0	X	0	1	X	0	0
0	1	1	1	1	0	0	1	0	0	1	0	1	0
1	0	0	0	1	0	1	X	0	0	X	1	0	0
1	0	0	1	1	0	0	X	0	0	X	0	X	1
1	0	1	0	0	0	1	0	1	0	X	X	0	0
1	0	1	1	1	0	0	X	0	0	X	0	1	1



Given these                      Derive these

Unused state 000:

0	0	0	0	X	X	X	X	X	X	X	X	X	X
0	0	0	1	X	X	X	X	X	X	X	X	X	X

 
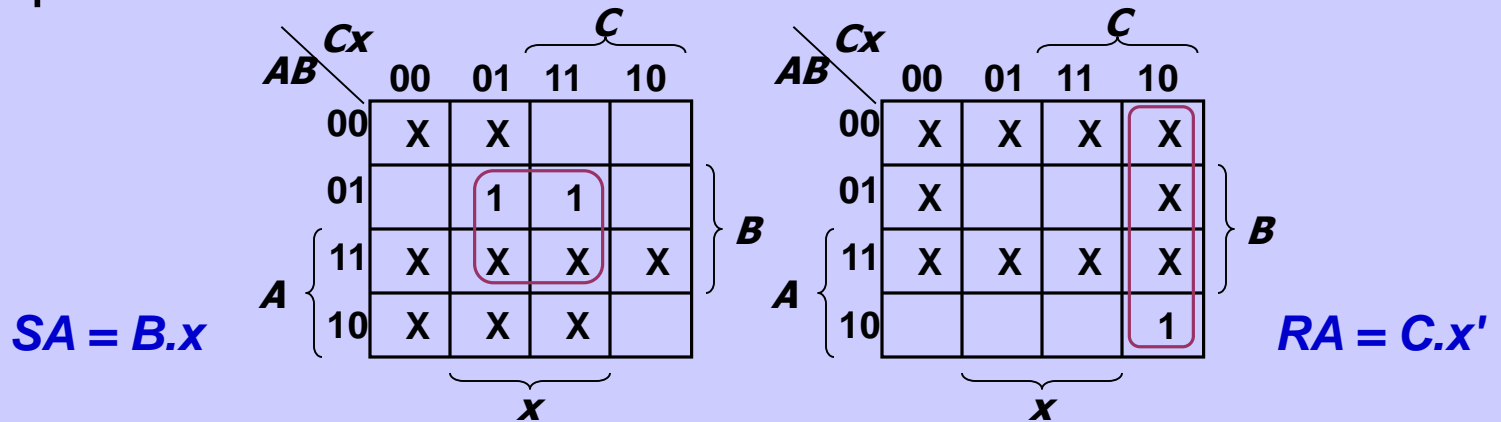
# Design: Example #3

- From state table, obtain expressions for flip-flop inputs.


 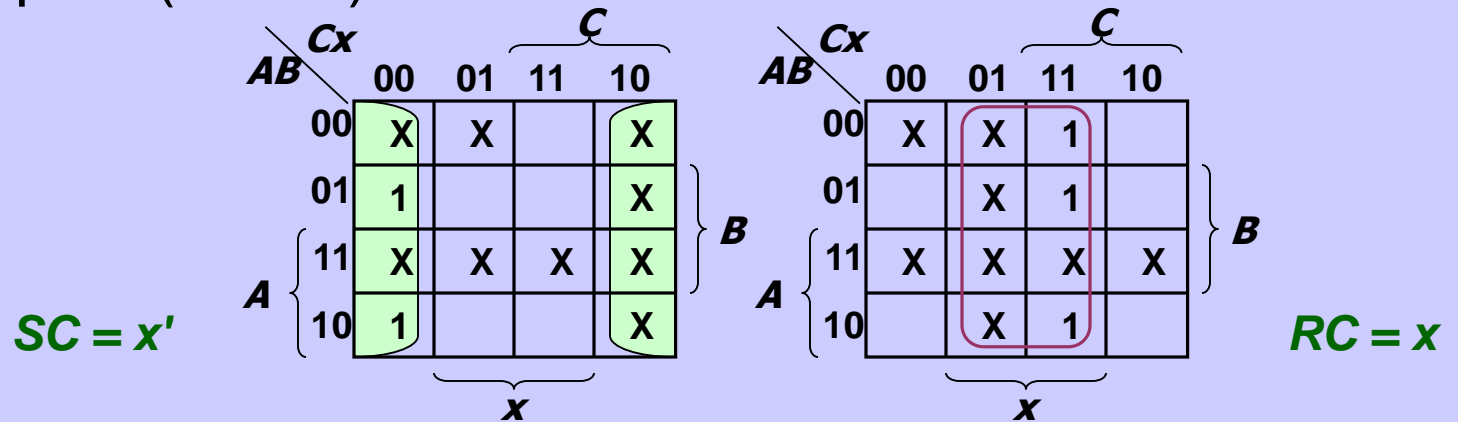
# Design: Example #3

- From state table, obtain expressions for flip-flop inputs (cont'd).




- $$y = A.x$$


 
# Design of Synchronous Counters

- **Counter**: a sequential circuit that cycles through a sequence of states.
- **Binary counter**: follows the *binary sequence*. An  $n$ -bit binary counter (with  $n$  flip-flops) counts from 0 to  $2^n - 1$ .
- Example 1: A 3-bit binary counter (using T flip-flops).






Present state			Next state			Flip-flop inputs		
$A_2$	$A_1$	$A_0$	$A_2^+$	$A_1^+$	$A_0^+$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1



# Design of Synchronous Counters

- 3-bit binary counter (cont'd).

Present state			Next state			Flip-flop inputs		
$A_2$	$A_1$	$A_0$	$A_2^+$	$A_1^+$	$A_0^+$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

   


# Design of Synchronous Counters

- 3-bit binary counter (cont'd).

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$


$$TA_0 = 1$$

 

# Design of Synchronous Counters

 - Example 2: Counter with non-binary sequence:

000  $\rightarrow$  001  $\rightarrow$  010  $\rightarrow$  100  $\rightarrow$  101  $\rightarrow$  110 and back to 000



Present state			Next state			Flip-flop inputs					
A	B	C	A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

$$JA = B$$

$$KA = B$$

$$JB = C$$

$$KB = 1$$

$$JC = B'$$

$$KC = 1$$

# Design of Synchronous Counters

- Counter with non-binary sequence (cont'd).

$$JA = B$$



$$KA = B$$

$$JB = C$$

$$KB = 1$$

$$JC = B'$$

$$KC = 1$$

  

# Summary

- Sequential circuits have memory and they are more powerful than combinational circuits.
- Analyzing sequential circuits
  - ❖ Flip-flop characteristic table
  - ❖ State Table
  - ❖ State diagram
- Designing sequential circuits
  - ❖ Flip-flop excitation table
  - ❖ State assignment
  - ❖ Circuit output function
  - ❖ Flip-flop input function



# ◆ Finite State Machine (FSM)

- This is what we have been waiting for in this class. Using combinational and sequential logics, now you can design a lot of clever digital logic circuits for functional products. We will learn different steps you take to go from word problems to logic circuits. We first talk about a simplified version of FSM which is a counter.

## ◆ Moore/Mealy machines

- There are two different ways to express the FSMs with respect to the output. Both have different advantages so it is good to know them.

# Finite state machines: more than counters

---

- ◆ FSM: A system that visits a **finite** number of logically distinct states
- ◆ Counters are simple FSMs
  - Outputs and states are identical
  - Visit states in a fixed sequence without inputs
- ◆ FSMs are typically more complex than counters
  - Outputs can depend on current state and on inputs
  - State sequencing depends on current state and on inputs

# FSM design

## ■ Counter-design procedure

- 1.State diagram
- 2.State-transition table
- 3.Next-state logic minimization
- 4.Implement the design

## ■ FSM-design procedure


- 1.State diagram
- 2.state-transition table
- 3.State minimization
- 4.State encoding
- 5.Next-state logic minimization
- 6.Implement the design


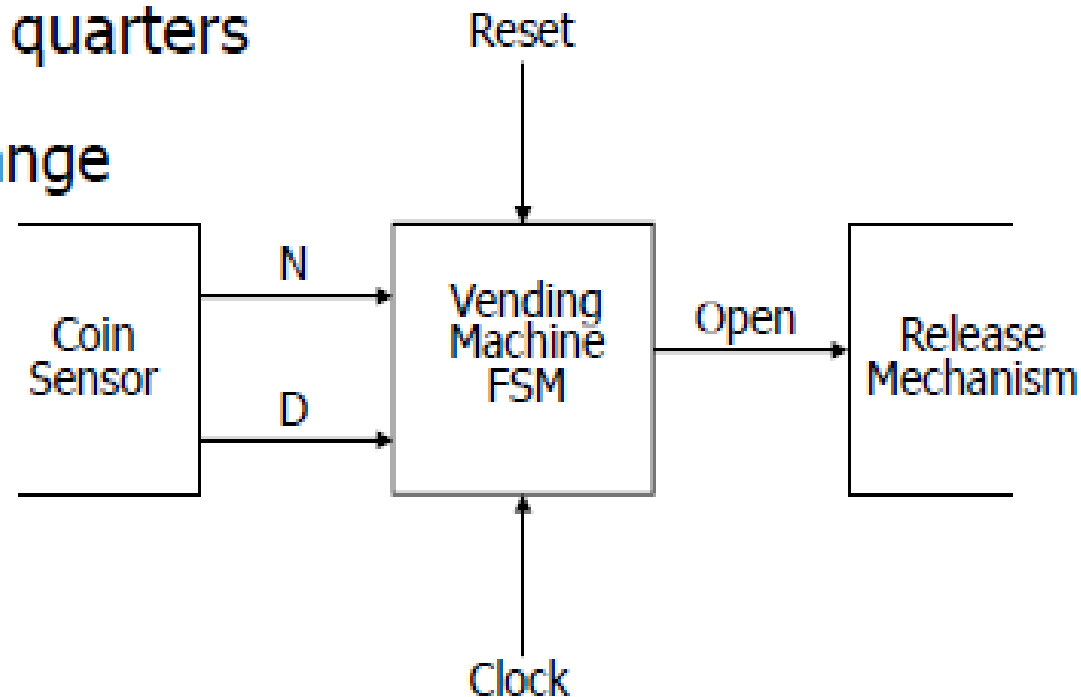
# Example: A vending machine

---


- ◆ 15 cents for a cup of coffee
- ◆ Doesn't take pennies or quarters
- ◆ Doesn't provide any change



- **FSM-design procedure**

1. State diagram
2. state-transition table
3. State minimization
4. State encoding
5. Next-state logic minimization
6. Implement the design
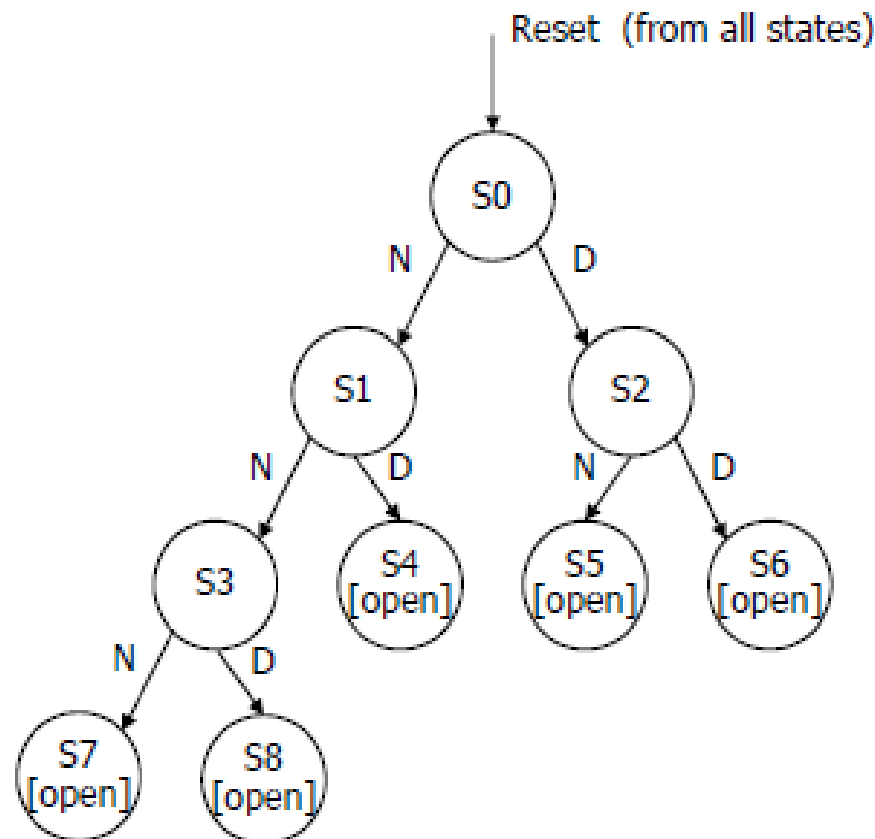
# A vending machine: (conceptual) state diagram



Draw self-loops for  
 $N' + D'$  for S0 to S3


Also draw self-loops for  
1 for S4 to S8

# A vending machine: State transition table


present state	inputs		next state	output open
	D	N		
S0	0	0	S0	0
	0	1	S1	0
	1	0	S2	0
	1	1	X	X
S1	0	0	S1	0
	0	1	S3	0
	1	0	S4	0
	1	1	X	X
S2	0	0	S2	0
	0	1	S5	0
	1	0	S6	0
	1	1	X	X
S3	0	0	S3	0
	0	1	S7	0
	1	0	S8	0
	1	1	X	X
S4	X	X	S4	1
S5	X	X	S5	1
S6	X	X	S6	1
S7	X	X	S7	1
S8	X	X	S8	1
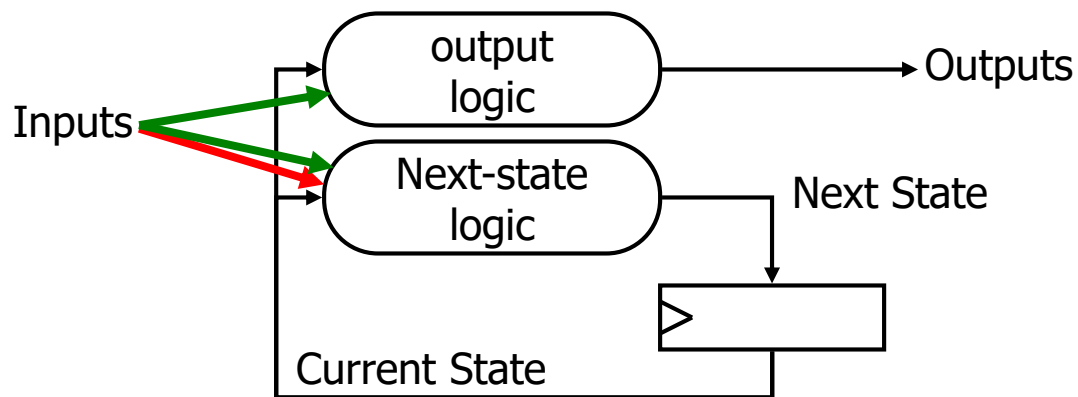
# Generalized FSM model: Moore and Mealy

- ◆ Combinational logic computes next state and outputs
  - Next state is a function of current state and inputs
  - Outputs are functions of
    - ⚡ Current state (**Moore** machine)
    - ⚡ Current state and inputs (**Mealy** machine)




# Moore versus Mealy machines

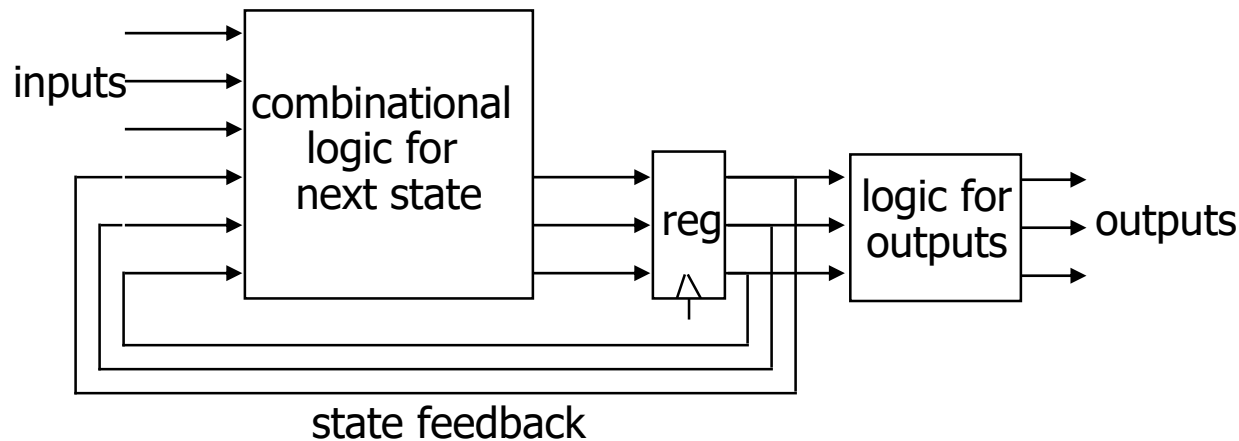
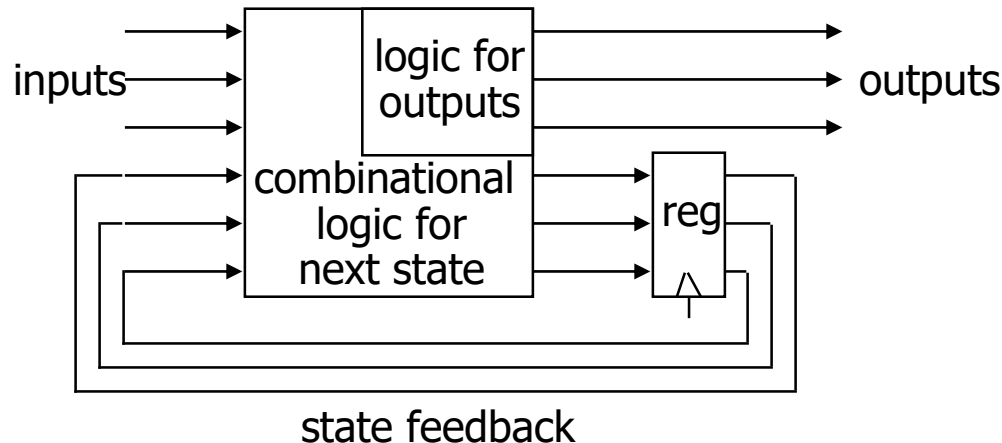
## Moore machine

Outputs are a function of current state

Outputs change synchronously with state changes



## Mealy machine

Outputs depend on state **and** on inputs

Input changes can cause immediate output changes  
**(asynchronous)**

# Impacts start of the FSM design procedure

- Counter-design procedure

1. State diagram
2. State-transition table
3. Next-state logic minimization
4. Implement the design

- FSM-design procedure

1. State diagram
2. State-transition table
3. State minimization
4. State encoding
5. Next-state logic minimization
6. Implement the design

# State Diagrams

- ◆ Moore machine

- Each state is labeled by a pair:

state-name/output    or    state-name [output]



- ◆ Mealy machine

- Each transition arc is labeled by a pair:

input-condition/output
  
# Example 10 $\rightarrow$ 01: Moore or Mealy?


- ◆ Circuits recognize  $AB=10$  followed by  $AB=01$ 
  - What kinds of machines are they?




 
# Example “01 or 10” detector: a Moore machine


- ◆ Output is a function of state only
  - Specify output in the state bubble



reset	input	current state	next state	current output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1
 
# Example “01 or 10” detector: a Mealy machine

- ◆ Output is a function of state and inputs
  - Specify outputs on transition arcs



reset	input	current state	next state	current output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

# Comparing Moore and Mealy machines

## ◆ Moore machines

- + Safer to use because outputs change at clock edge
- May take additional logic to decode state into outputs

## ◆ Mealy machines

- + Typically have fewer states
- + React faster to inputs — don't wait for clock
- Asynchronous outputs can be dangerous


## ◆ We often design synchronous Mealy machines

- Design a Mealy machine
- Then register the outputs

# Synchronous (registered) Mealy machine
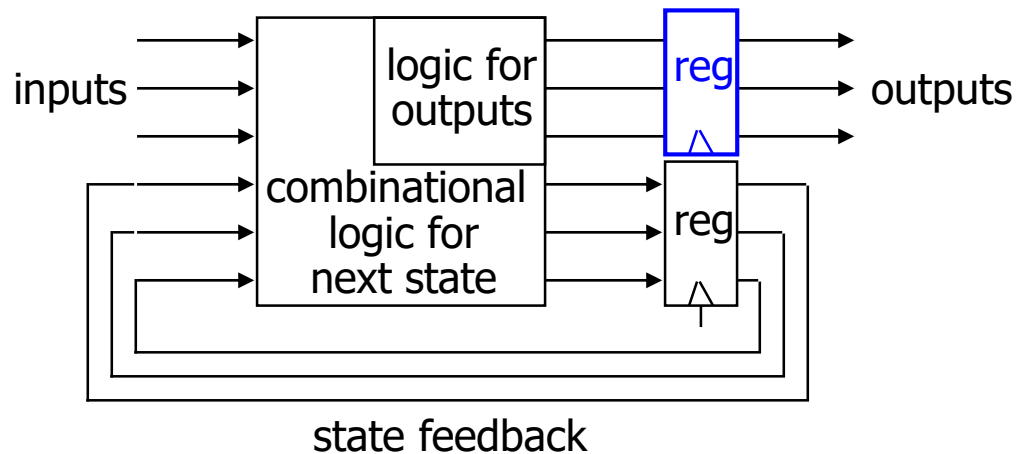
## ◆ Registered state and registered outputs


- No glitches on outputs
- No race conditions between communicating machines




# Example “=01”: Moore or Mealy?

## ◆ Recognize $AB = 01$

### ■ Mealy or Moore?

 

Registered Mealy  
(actually Moore)

 


# Example: A parity checker

- ◆ Serial input string
  - $OUT=1$  if odd # of 1s in input
  - $OUT=0$  if even # of 1s in input
- ◆ Let's do this for Moore and Mealy


# Example: A parity checker

## 1. State diagram

Moore

 

Mealy

 

# Example: A parity checker

## 1. State-transition table

Moore

Present State	Input	Next State	Present Output
Even	0	Even	0
Even	1	Odd	0
Odd	0	Odd	1
Odd	1	Even	1

Mealy

Present State	Input	Next State	Present Output
Even	0	Even	0
Even	1	Odd	1
Odd	0	Odd	1
Odd	1	Even	0



# Example: A parity checker

## 3. State minimization: Already minimized

- Need both states (even and odd)
- Use one flip-flop

# Example: A parity checker

## 4. State encoding

Moore

Present State	Input	Next State	Present Output
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	1

Assignment

Even 0

Odd 1

Mealy

Present State	Input	Next State	Present Output
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0


# Example: A parity checker

## 5. Next-state logic minimization


- Assume D flip-flops
- Next state = (present state) XOR (present input)

## 6. Implement the design

Moore

 

Mealy

 

# What was covered so far on FSM

- ◆ Finite state machines
  - FSM design procedure
    1. State diagram
    2. State-transition table
    3. State minimization
    4. State encoding
    5. Next-state logic minimization
    6. Implement the design
  - No Mealy machines