

CSE1003

Problems

Design a logic circuit that has three inputs, A , B , and C , and whose output will be HIGH only when a majority of the inputs are HIGH.

Step 1. Set up the truth table.

A	B	C	x
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Step 2. Write the AND term for each case where the output is a 1.


Step 3. Write the sum-of-products expression for the output.

$$x = \overline{A}\overline{B}C + A\overline{B}C + A\overline{B}\overline{C} + ABC$$


Step 4. Simplify the output expression.

$$x = BC + AC + AB$$

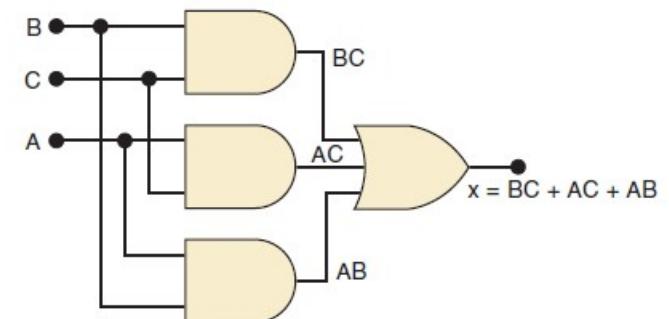Step 5. Implement the circuit for the final expression.



- In a simple copy machine, a stop signal, S , is to be generated to stop the machine operation and energize an indicator light whenever either of the following conditions exists: (1) there is no paper in the paper feeder tray; or (2) the two microswitches in the paper path are activated, indicating a jam in the paper path. The presence of paper in the feeder tray is indicated by a HIGH at logic signal P . Each of the microswitches produces a logic signal (Q and R) that goes HIGH whenever paper is passing over the switch to activate it. Design the logic circuit to produce a HIGH at output signal S for the stated conditions, and implement it using the 74HC00 CMOS quad two-input NAND chip.

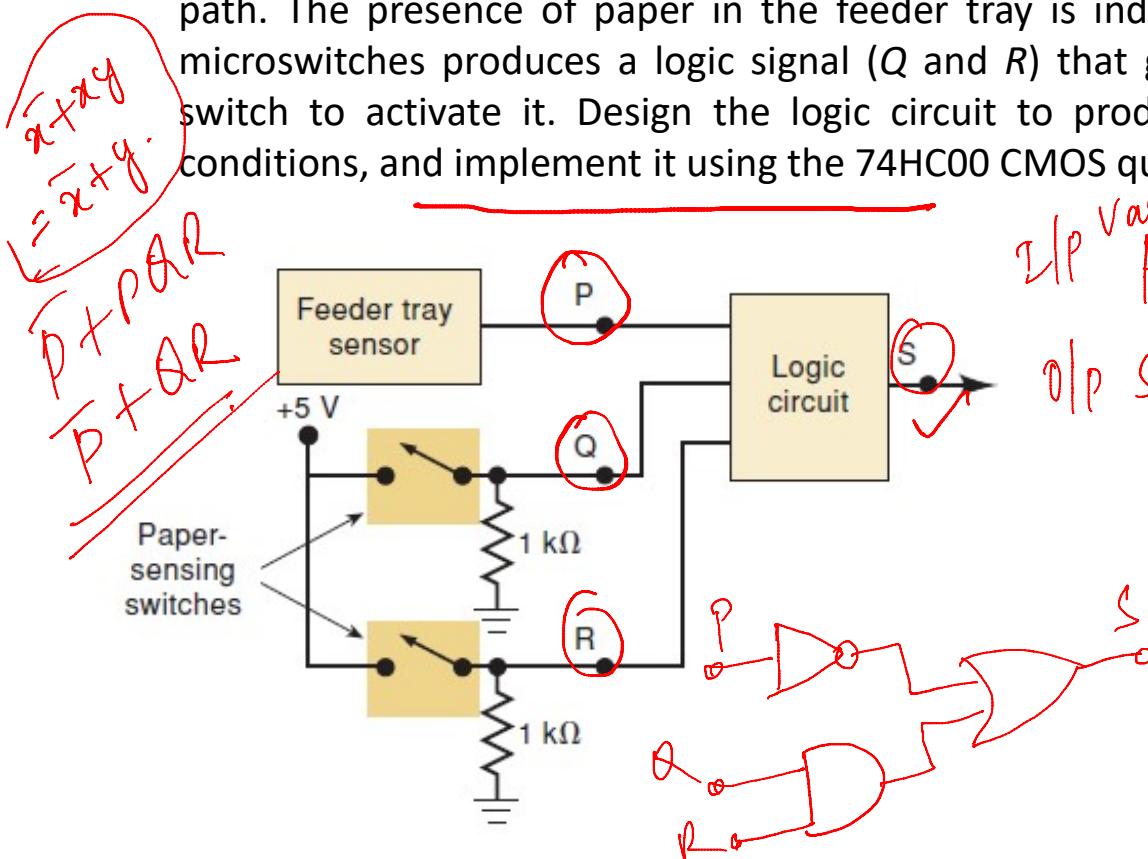

2/p variables
D/P S

P	Q	R	S
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$\begin{aligned} P &= 0 \\ Q &= 1 \\ R &= 1 \end{aligned}$$




$$S = \overline{P} \overline{Q} \overline{R} + \overline{P} \overline{Q} R + \overline{P} Q \overline{R}$$

$$+ \overline{P} Q R + P \overline{Q} R$$


$$+ P Q R$$

Simplified Boolean expression
Simplified expression

$$S = \overline{P} + Q R$$

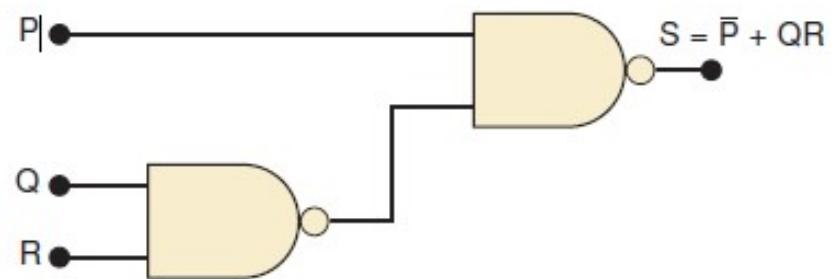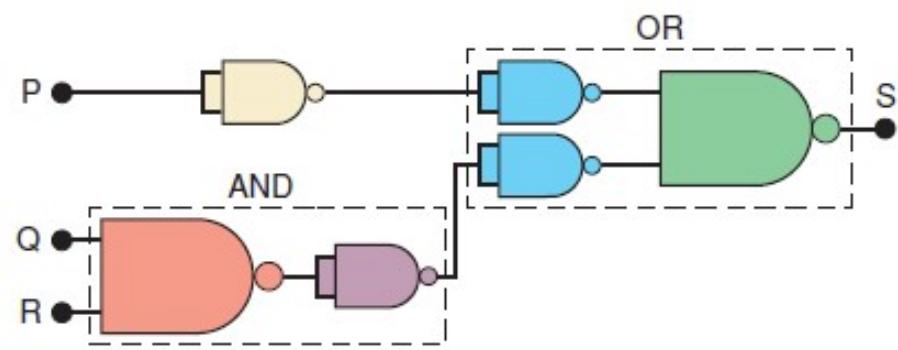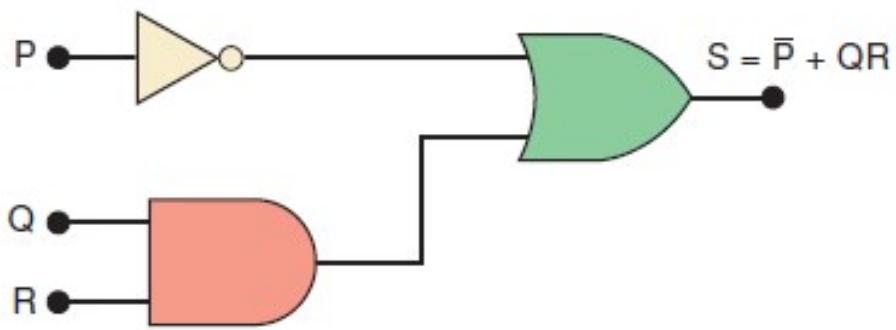

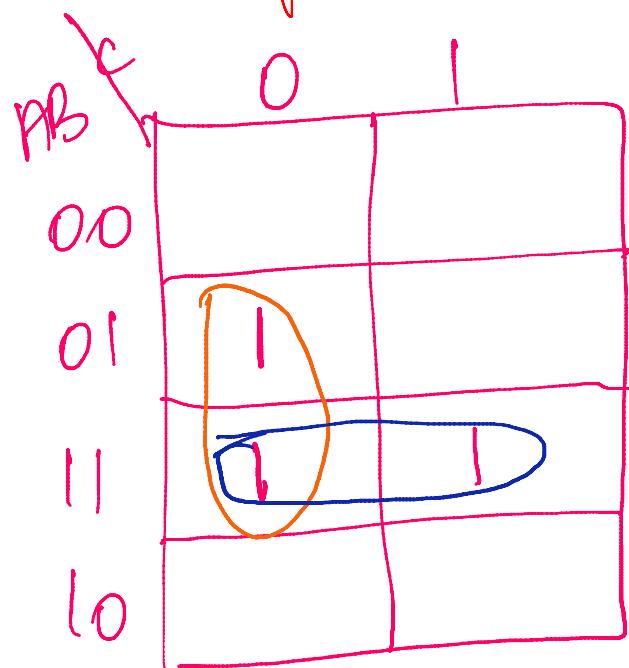Simplify $f = A'B'C' + ABC' + ABC$ using maxterms.
Using K-map method.




Using minterms

$$f = BC' + AB \text{ SOP form}$$

$$f = A'B'C' + AB'C' + ABC$$

010	110	111
-----	-----	-----

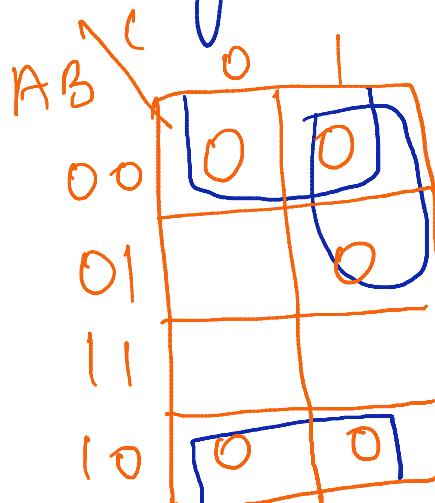Using maxterms - place 0's in the remaining squares



The group of 0's provide the complement of the function

$$\bar{F} = \bar{B} + \bar{A}C$$

$$F = \overline{\bar{F}} = \overline{\bar{B} + \bar{A}C} = \bar{B} (\bar{\bar{A}} + \bar{C})$$

$$f = B (A + \bar{C}) \quad \text{POS form}$$

Simplify the following Boolean function into SOP & POS forms.

$$F(A, B, C) = \Sigma(0, 1, 3, 4, 5)$$

Fill in 1's in the squares of minterms for which $F=1$
& fill in 0's in the remaining squares for which $F=0$

Group of 1's provide the SOP form

Group of 0's provide the complement of the function

$\bar{A} \bar{B} \bar{C}$	0	1
00	1	1
01	0	1
11	0	0
10	1	1

Group of 1's — SOP form

$$F = \overline{B} + \overline{A}C$$

Group of 0's — complement of F

$$\overline{F} = B\overline{C} + AB$$

$$F = \overline{\overline{F}} = \overline{B\overline{C} + AB} = \overline{B\overline{C}} \cdot \overline{AB}$$

$$= (\overline{B} + \overline{C}) \cdot (\overline{A} + \overline{B})$$

$$= (\overline{B} + C) (\overline{A} + \overline{B})$$

Give simplified logic equation of Table by QM method.

	A	B	C	Y
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	0
m_4	1	0	0	0
m_5	1	0	1	0
m_6	1	1	0	1
m_7	1	1	1	1

Stage 1

Minterms	Binary	Group
	A B C	
m_2	0 1 0	I
m_6	1 1 0	II
m_7	1 1 1	III

Stage 2

Minterms	Binary	A B C
2, 6	- 1 0	P1
6, 7	1 1 -	P2

Prime Implicant chart

	2	6	7
2, 6 P1	✓	✓	
6, 7 P2		✓	✓
EPI			
EP2			

$$Y = \underline{B \bar{C}} + \underline{\bar{A} B} =$$

