
Chapter 3 Ctd: Combinational Functions and Circuits


Value Fixing, Transferring, and Inverting

- Four different functions are possible as a function of single Boolean variable

TABLE 4-1
Functions of One Variable


X	F = 0	F = X	F = \bar{X}	F = 1
0	0	0	1	1
1	0	1	0	1

Transferring Inverting Value Fixing

 


Value Fixing for Implementing a Function

 - Y is actually a function of six variables - truth table with 64 rows and 7 clmns
- Putting $I_0 - I_3$ in the output column reduces the truth table



$$Y(A, B, I_0, I_1, I_2, I_3) = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$$

Value Fixing for Implementing a Function

 


16 different functions can be implemented by setting $I_0 - I_3$ appropriately

□ **TABLE 4-2**
Function Implementation by Value-Fixing

A	B	$Y = A + B$	$Y = A\bar{B} + \bar{A}B$	$Y = A + B$ ($I_3 = 1$) or $Y = A\bar{B} + \bar{A}B$ ($I_3 = 0$)
0	0	0	0	0
0	1	1	1	1
1	0	1	1	1
1	1	1	0	I_3

What is a decoder?

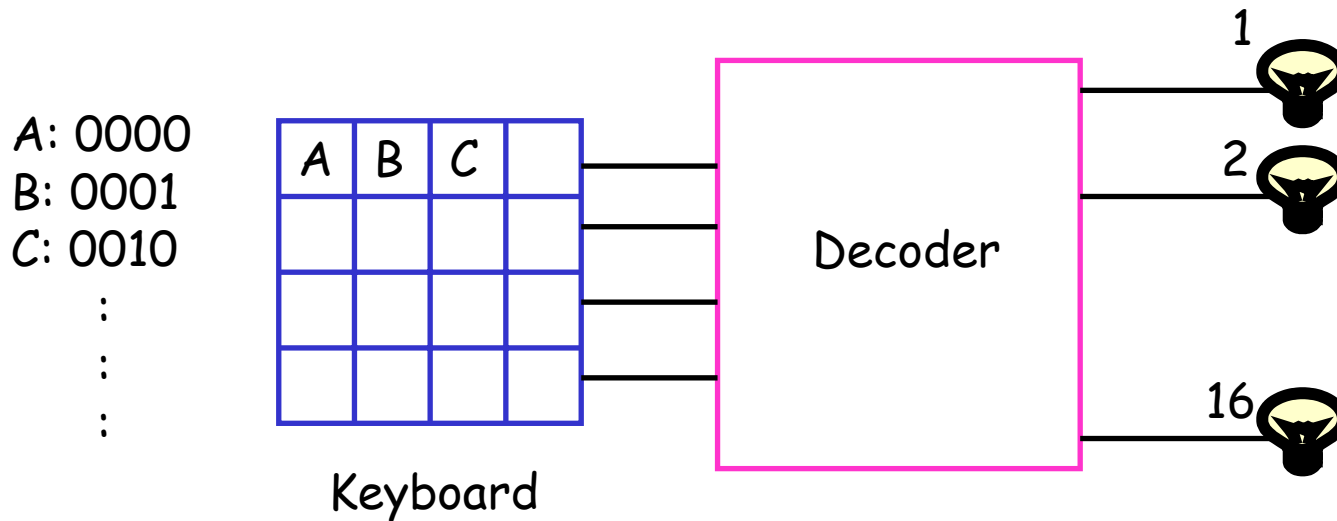


- Decoder: A combinational circuit with an n -bit binary code applied to its inputs and m -bit binary code appearing at the outputs
 - $n \leq m \leq 2^n$
 - Detect which of the 2^n combinations is represented at the inputs
 - Produce m outputs, only one of which is "1"

1-to-2 (Line) Decoder

A	D₀	D₁
0	1	0
1	0	1

(a)

 

(b)

2-to-4 Decoder

- A 2-to-4 decoder operates according to the following truth table
 - The 2-bit input is called S_1S_0 , and the four outputs are Q_0 - Q_3
 - If the input is the binary number i , then output Q_i is uniquely true

S_1	S_0	Q_0	Q_1	Q_2	Q_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- For instance, if the input $S_1 S_0 = 10$ (decimal 2), then output Q_2 is true, and Q_0 , Q_1 , Q_3 are all false
- This circuit “decodes” a binary number into a “one-of-four” code

How can you build a 2-to-4 decoder?

- Follow the design procedures from last time! We have a truth table, so we can write equations for each of the four outputs (Q0-Q3)

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- In this case there's not much to be simplified. Here are the equations:

$$Q0 = S1' S0'$$


$$Q1 = S1' S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

2-to-4 Decoder

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

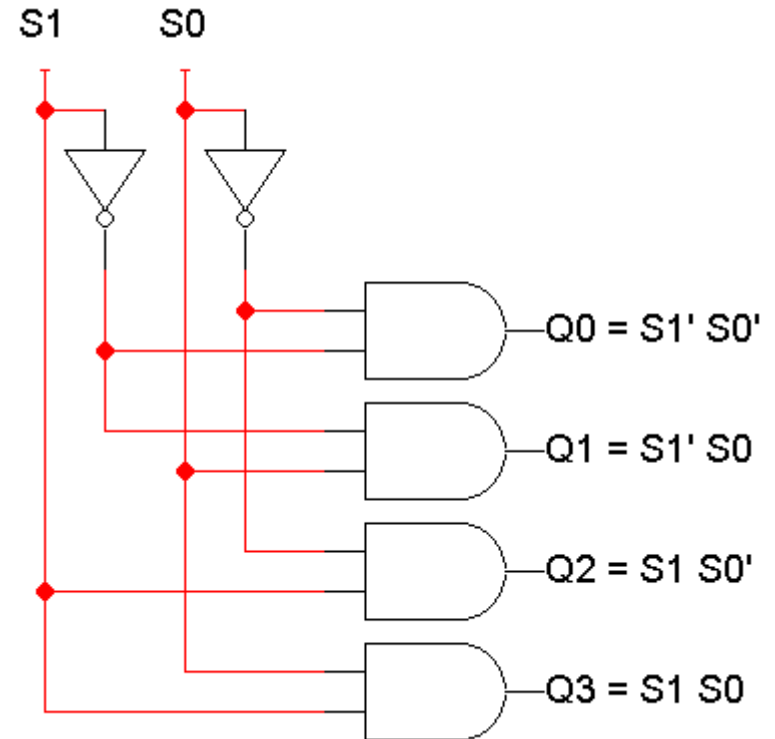

Enable Inputs

- Many devices have an additional **enable input**, which is used to "activate" or "deactivate" the device
- For a decoder,
 - EN=1 activates the decoder, so it behaves as specified earlier. Exactly one of the outputs will be 1
 - EN=0 "deactivates" the decoder. By convention, that means *all* of the decoder's outputs are 0
- We can include this additional input in the decoder's truth table:

EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

An aside: abbreviated truth tables

- In this table, note that whenever $EN=0$, the outputs are always 0, *regardless* of inputs $S1$ and $S0$.



EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

- We can abbreviate the table by writing x's in the input columns for $S1$ and $S0$

EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Blocks and Abstraction

  - Decoders are common enough that we want to encapsulate them and treat them as an individual entity
- Block diagrams** for 2-to-4 decoders are shown here. The *names* of the inputs and outputs, not their order, is what matters.




$$\begin{aligned} Q0 &= S1' S0' \\ Q1 &= S1' S0 \\ Q2 &= S1 S0' \\ Q3 &= S1 S0 \end{aligned}$$

- A decoder block provides **abstraction**:
 - You can use the decoder as long as you know its truth table or equations, without knowing exactly what's inside
 - It makes diagrams simpler by hiding the internal circuitry
 - It simplifies hardware reuse. You don't have to keep rebuilding the decoder from scratch every time you need it
- These blocks are like functions in programming!

3-to-8 decoder

 - Larger decoders are similar. Here is a 3-to-8 decoder
 - The block symbol is on the right
 - A truth table (without EN) is below
 - Output equations are at the bottom right
- Again, only one output is true for any input combination



S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Q0 = S2' S1' S0'$$

$$Q1 = S2' S1' S0$$

$$Q2 = S2' S1 S0'$$

$$Q3 = S2' S1 S0$$

$$Q4 = S2 S1' S0'$$

$$Q5 = S2 S1' S0$$

$$Q6 = S2 S1 S0'$$

$$Q7 = S2 S1 S0$$

So what good is a decoder?

- Do the truth table and equations look familiar?

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$Q0 = S1' S0'$$

$$Q1 = S1' S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

- Decoders are sometimes called **minterm generators**
 - For each of the input combinations, exactly one output is true
 - Each output equation contains all of the input variables
 - These properties hold for all sizes of decoders
- Arbitrary functions can be implemented with decoders. If a sum of minterms equation for a function is given, a decoder (a minterm generator) is used to implement that function

Design example: Addition

- Let's make a circuit that adds three 1-bit inputs X , Y and Z
- We will need two bits to represent the total; let's call them C and S , for "carry" and "sum." Note that C and S are two separate functions of the same inputs X , Y and Z
- Here are a truth table and sum-of-minterms equations for C and S

$0 + 1 + 1 = 10$ →



X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

← $1 + 1 + 1 = 11$

$C(X,Y,Z) = \sum m(3,5,6,7)$
 $S(X,Y,Z) = \sum m(1,2,4,7)$


Decoder-based Adder

  - Here, two 3-to-8 decoders implement C and S as sums of minterms.



Using just one decoder

 - Since the two functions C and S both have the same inputs, we could use just one decoder instead of two.



Building a 3-to-8 decoder

- You could build a 3-to-8 decoder directly from the truth table and equations below, just like how we built the 2-to-4 decoder
- Another way to design a decoder is to break it into smaller pieces
- Notice some patterns in the table below:
 - When $S_2 = 0$, outputs Q_0 - Q_3 are generated as in a 2-to-4 decoder
 - When $S_2 = 1$, outputs Q_4 - Q_7 are generated as in a 2-to-4 decoder

S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Q_0 = S_2' S_1' S_0' = m_0$$

$$Q_1 = S_2' S_1' S_0 = m_1$$

$$Q_2 = S_2' S_1 S_0' = m_2$$

$$Q_3 = S_2' S_1 S_0 = m_3$$

$$Q_4 = S_2 S_1' S_0' = m_4$$


$$Q_5 = S_2 S_1' S_0 = m_5$$

$$Q_6 = S_2 S_1 S_0' = m_6$$

$$Q_7 = S_2 S_1 S_0 = m_7$$

Decoder Expansion

 
- You can use enable inputs to string decoders together. Here's a 3-to-8 decoder constructed from two 2-to-4 decoders:



S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


Modularity

 - Be careful not to confuse the "inner" inputs and outputs of the 2-to-4 decoders with the "outer" inputs and outputs of the 3-to-8 decoder (which are in boldface)
- This is similar to having several functions in a program which all use a formal parameter "x"




A variation of the standard decoder

 - The decoders we've seen so far are **active-high** decoders



EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 
- An **active-low decoder** is the same thing, but with an inverted EN input and inverted outputs




EN'	S1'	S0'	Q0'	Q1'	Q2'	Q3'
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1

Separated at birth?

 - Active-high decoders generate *minterms*, as we've already seen



 
- The output equations for an active-low decoder are mysteriously similar, yet somehow different



- It turns out that active-low decoders generate *maxterms*

Active-low Decoder

 - So we can use active-low decoders to implement arbitrary functions too, but as a product of maxterms
- For example, here is an implementation of the function $f(x,y,z) = \prod M(4,5,7)$ using an active-low decoder




- The "ground" symbol connected to EN represents logical 0, so this decoder is always enabled

Summary of Decoders

- A n -to- 2^n decoder generates the minterms of an n -variable function
 - As such, decoders can be used to implement arbitrary functions
 - Later on we'll see other uses for decoders too
- Some variations of the basic decoder include:
 - Adding an enable input
 - Using active-low inputs and outputs to generate maxterms
- We also talked about:
 - Applying our circuit analysis and design techniques to understand and work with decoders
 - Using block symbols to encapsulate common circuits like decoders
 - Building larger decoders from smaller ones

Encoder

 - An encoder is a digital function that performs the inverse operation of a decoder
- **Octal-to-Binary Encoder:** This encoder has eight inputs, one for each of the octal digits, and three outputs that generate the corresponding binary number
 - Only one input can have the value of 1 at any given time



Octal-to-Binary Encoder

□ **TABLE 4-4**
Truth Table for Octal-to-Binary Encoder

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7,$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$



Priority Encoder

- A priority encoder is a combinational circuit that implements a priority function
- Octal-to-Binary: If more than one input is active simultaneously, the output produces an incorrect combination
- Priority Encoder: If two or more inputs are active simultaneously, the input having the highest priority takes precedence


□ **TABLE 4-5**
Truth Table of Priority Encoder

Inputs				Outputs		
D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

4-Input Priority Encoder

  


4-Input Priority Encoder

 


Multiplexers

 - Multiplexers, or muxes, are used to choose between resources
- A real-life example: in the old days before networking, several computers could share one printer through the use of a switch.



Multiplexers

 
- A **2^n -to-1 multiplexer** sends one of 2^n input lines to a single output line
 - A multiplexer has two sets of *inputs*:
 - 2^n **data input** lines
 - n **select** lines, to pick one of the 2^n data inputs
 - The mux *output* is a single bit, which is one of the 2^n data inputs
- The simplest example is a 2-to-1 mux:



- The select bit S controls which of the data bits $D0$ - $D1$ is chosen:
 - If $S=0$, then $D0$ is the output ($Q=D0$).
 - If $S=1$, then $D1$ is the output ($Q=D1$).

More truth table abbreviations

 - Here is a full truth table for this 2-to-1 mux, based on the equation:




S	D1	D0	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Here is another kind of abbreviated truth table
 - Input variables appear in the output column
 - This table implies that when $S=0$, the output $Q=D0$, and when $S=1$ the output $Q=D1$
 - This is a pretty close match to the equation

S	Q
0	D0
1	D1

2-to-1 Mux

 

4-to-1 Mux

□ **TABLE 4-7**
Condensed Truth Table for 4-to-1-Line Multiplexer


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$Y = (S_1'S_0')I_0 + (S_1'S_0)I_1 + (S_1S_0')I_2 + (S_1S_0)I_3$$


Decoder



4-to-1 Mux

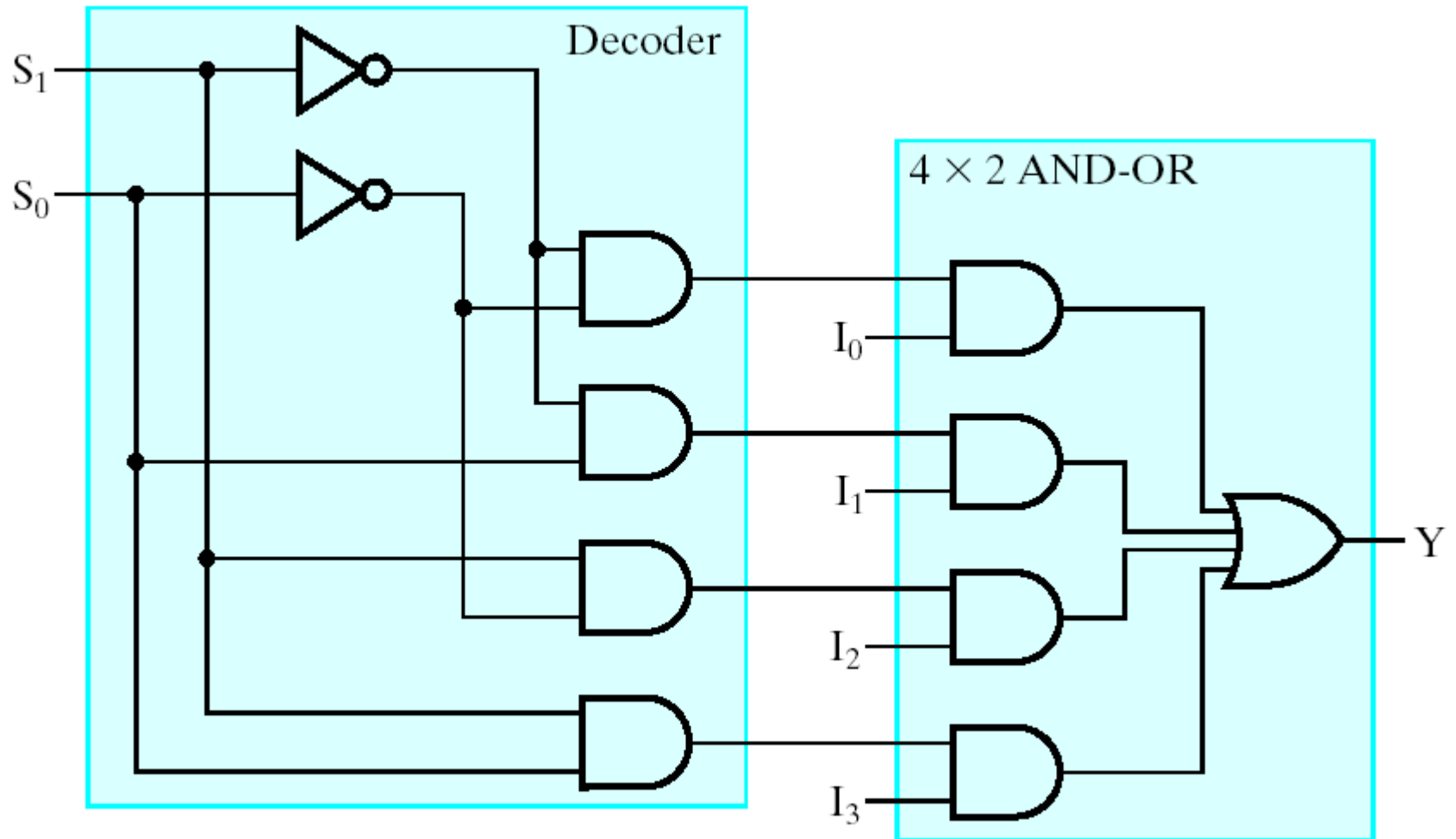


4-to-1 Mux with Enable Input

 

EN	S1	S0	Q
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	x	x	1

$$Q = EN'S1'S0'D0 + EN'S1'S0D1 + EN'S1S0'D2 + EN'S1S0D3 + EN$$


Quad 4-to-1 Mux

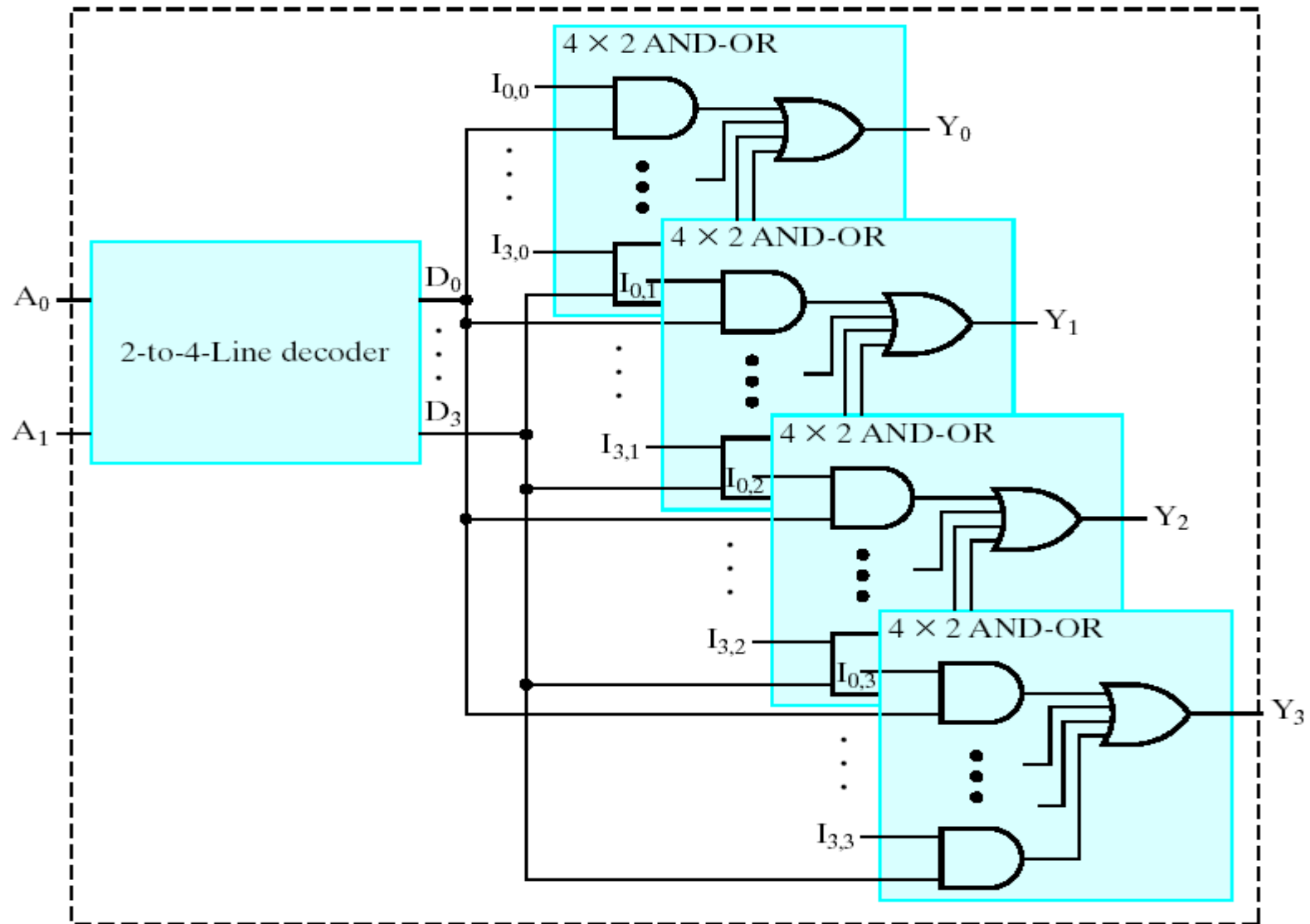

Implementing functions with multiplexers

- Muxes can be used to implement arbitrary functions
- One way to implement a function of n variables is to use an 2^n -to-1 mux:
 - For each minterm m_i of the function, connect 1 to mux data input D_i . Each data input corresponds to one row of the truth table
 - Connect the function's input variables to the mux select inputs. These are used to indicate a particular input combination
- For example, let's look at $f(x,y,z) = \Sigma m(1,2,6,7)$.


x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

A more efficient way

- We can actually implement $f(x,y,z) = \sum m(1,2,6,7)$ with just a 4-to-1 mux, instead of an 8-to-1
- Step 1: Find the truth table for the function, and group the rows into pairs. Within each pair of rows, x and y are the same, so f is a function of z only.
 - When $xy=00$, $f=z$
 - When $xy=01$, $f=z'$
 - When $xy=10$, $f=0$
 - When $xy=11$, $f=1$
- Step 2: Connect the first two input variables of the truth table (here, x and y) to the select bits $S1$ $S0$ of the 4-to-1 mux.
- Step 3: Connect the equations above for $f(z)$ to the data inputs $D0$ - $D3$.


x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Example: multiplexer-based adder

- Let's implement the adder carry function, $C(X,Y,Z)$, with muxes
- There are three inputs, so we'll need a 4-to-1 mux
- The basic setup is to connect two of the input variables (usually the first two in the truth table) to the mux select inputs

X	Y	Z	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

With $S1=X$ and $S0=Y$, then

$$Q = X'Y'D0 + X'YD1 + XY'D2 + XYD3$$

Multiplexer-based carry

- We can set the multiplexer data inputs D0-D3, by fixing X and Y and finding equations for C in terms of just Z.


X	Y	Z	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

When XY=00, C=0

When XY=01, C=Z

When XY=10, C=Z

When XY=11, C=1

 

$$\begin{aligned}
 C &= X' Y' D0 + X' Y D1 + X Y' D2 + X Y D3 \\
 &= X' Y' 0 + X' Y Z + X Y' Z + X Y 1 \\
 &= X' Y Z + X Y' Z + XY \\
 &= \Sigma m(3,5,6,7)
 \end{aligned}$$

Multiplexer-based sum

- Here's the same thing, but for the sum function $S(X,Y,Z)$


X	Y	Z	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

When $XY=00$, $S=Z$

When $XY=01$, $S=Z'$

When $XY=10$, $S=Z'$


When $XY=11$, $S=Z$

 

$$\begin{aligned} S &= X' Y' D0 + X' Y D1 + X Y' D2 + X Y D3 \\ &= X' Y' Z + X' Y Z' + X Y' Z' + X Y Z \\ &= \Sigma m(1,2,4,7) \end{aligned}$$


Dual multiplexer-based full adder

 - We need *two* separate 4-to-1 muxes: one for C and one for S
- But sometimes it's convenient to think about the adder output as being a single 2-bit number, instead of as two separate functions
- A **dual 4-to-1 mux** gives the illusion of 2-bit data inputs and outputs
 - It's really just two 4-to-1 muxes connected together




Dual muxes in more detail

 
- You can make a dual 4-to-1 mux by connecting two 4-to-1 muxes. ("Dual" means "two-bit values.")
- In the diagram on the right, we're using S_1 - S_0 to choose one of the following *pairs* of inputs:
 - $2D_3$ $1D_3$, when S_1 $S_0 = 11$
 - $2D_2$ $1D_2$, when S_1 $S_0 = 10$
 - $2D_1$ $1D_1$, when S_1 $S_0 = 01$
 - $2D_0$ $1D_0$, when S_1 $S_0 = 00$




Selecting based on 3-state buffers

 

(a)

 

Selecting based on TGs

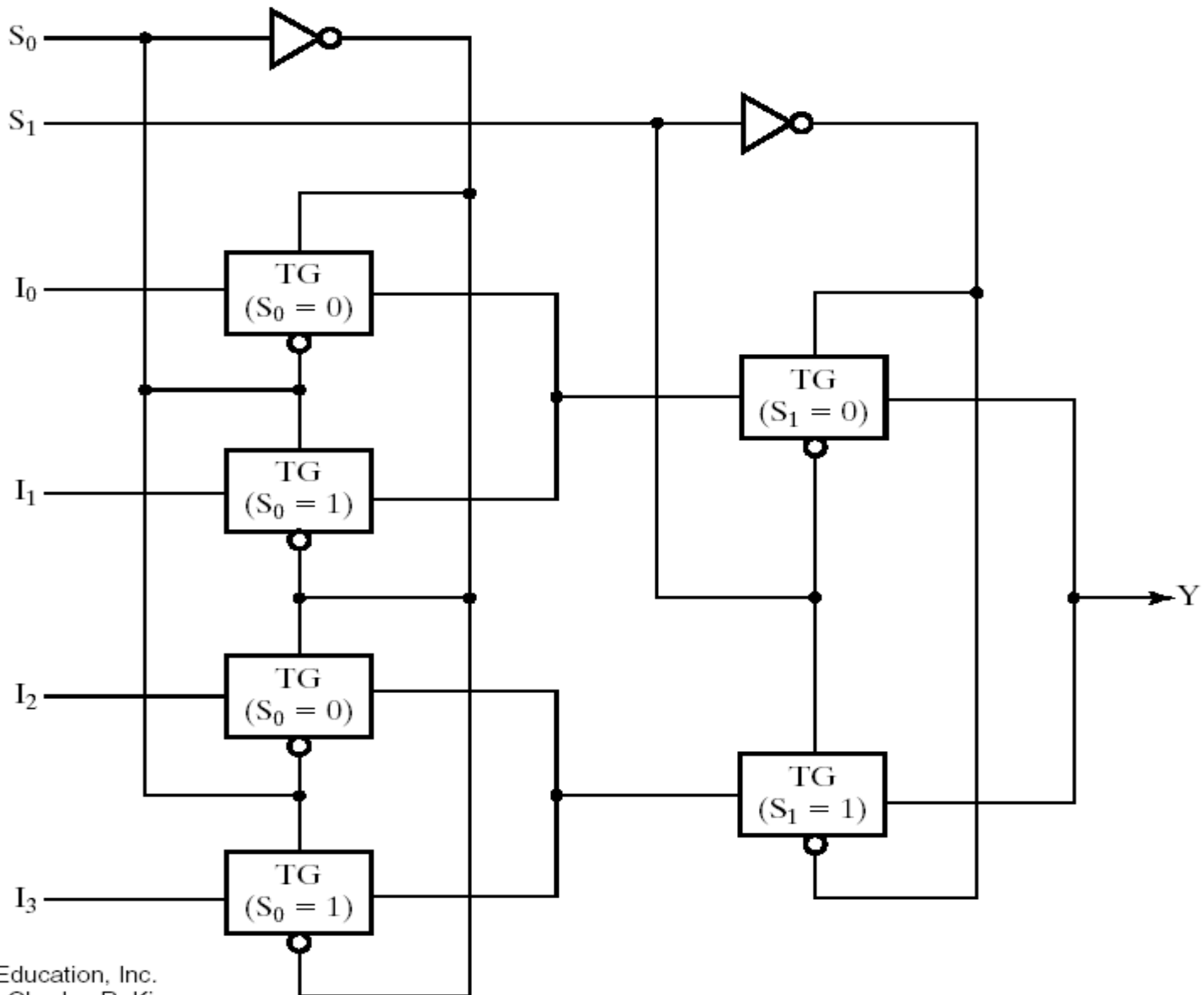

Summary of Muxes

- A 2^n -to-1 multiplexer routes one of 2^n input lines to a single output line
- Just like decoders,
 - Muxes are common enough to be supplied as stand-alone devices for use in modular designs.
 - Muxes can implement arbitrary functions
- We saw some variations of the standard multiplexer:
 - Smaller muxes can be combined to produce larger ones
 - We can add active-low or active-high enable inputs
- As always, we use truth tables and Boolean algebra to analyze things