

DATE: 2021/02/04

CLEAN ENERGYApparatus Required:

- Solar Cell (p-n junction diode)
- Light Source (100 W bulb)
- Ammeter
- Voltmeter
- Load Circuit
- Connecting Wires

SLO:

- To draw the I-V characteristics of a solar cell and to find out the efficiency and fill factor.

The maximum power generated $P_{max} = I_{mp} V_{mp}$ (where I_{mp} and V_{mp} are the current and voltage corresponding to maximum power).

$$FF = \frac{V_{mp} I_{mp}}{V_{oc} I_{sc}}$$

$$\eta = \frac{P_{max}}{A_c \cdot I} \quad (\text{where, } A_c \rightarrow \text{Area of solar cell} \\ I \rightarrow \text{Incident Intensity}).$$

DATE: 2021/02/04

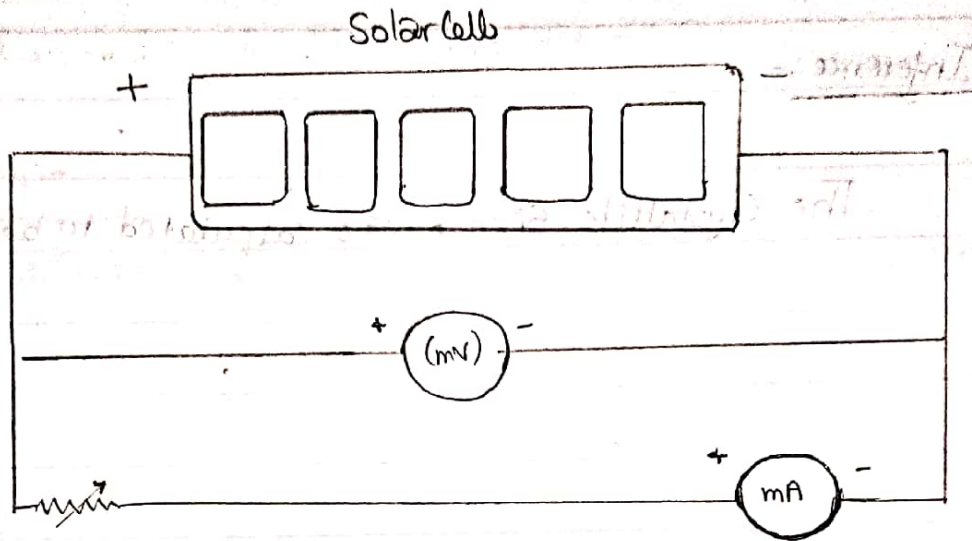


Fig:- Experimental Arrangement of Circuit

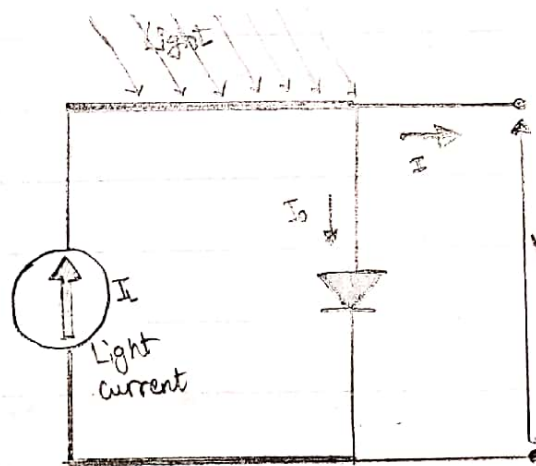


Fig:- Solar Cell

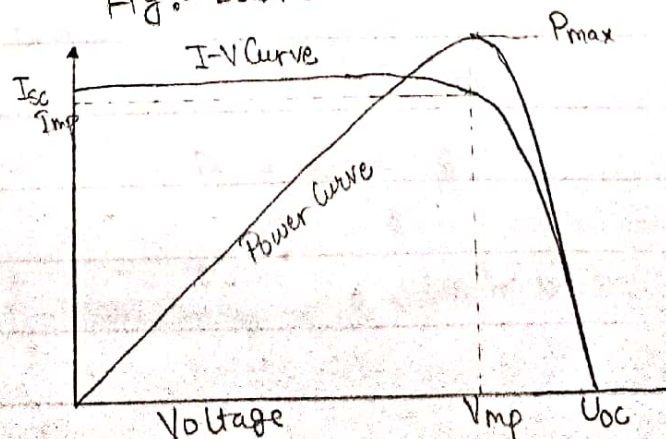


Fig:- Nature of Curve of I and P vs V.

Date: - 2021/02/04

Table: - IV characteristics

Distance (x) = 7cm Intensity of light = 217 W/m^2 Area of the solar cell = $22.75 \times 10^{-4} \text{ m}^2$			$I_{sc} = 14 \text{ mA}$ $V_{oc} = 1.74 \text{ V}$
Load Resistance (ohms)	Current (mA)	Voltage (V)	Power (mW)
10	14	0	0
22	14	0.15	2.1
33	14	0.35	4.9
47	14	0.7	9.8
68	14	0.85	11.9
82	12	0.9	10.8
100	12	1.15	13.8
150	10	1.3	13
220	7	1.5	10.5
470	3	1.6	4.8

Calculation: -

$$\text{Fill factor (FF)} = \frac{V_{mp} I_{mp}}{V_{oc} I_{sc}}$$

$$= \frac{1.15 \times 11.8 \times 10^{-3}}{14 \times 10^{-3} \times 1.74}$$

$$= 0.557$$

$$\text{Efficiency } (\eta) = \frac{P_{max}}{A \cdot I} = \frac{1.357 \times 10^{-2}}{22.75 \times 10^{-4} \times 217}$$

$$= 0.0275$$

$$= 2.7\%$$

Date: - 2021/02/04

Observations :-

1). For distance ($x_1 = 7\text{cm} = 7 \times 10^{-2}\text{m}$)

$$I_{mp} = 11.8\text{mA} = 11.8 \times 10^{-3}\text{A}$$

$$V_{mp} = 1.15\text{Volts}$$

$$P_{max} = I_{mp} \times V_{mp} = 11.8 \times 1.15 \times 10^{-3} = 13.57 \times 10^{-2}$$

$$\eta = 217\text{Wm}^{-2}$$

$$A_c = 22.75 \times 10^{-4}\text{m}^2$$

Results:

I-V characteristics of the solar cell were studied and the maximum power generated; FF and efficiency were calculated for two different source-cell distances.

For, $x_1 = 0.07\text{m}$

$$\text{Efficiency, } \eta = 2.75\%$$


$$FF = 0.557$$

Along Voltage axis, 10 small divisions = 0.2 Volt
Along Current axis, 10 small divisions = 1mA
Along power axis, 10 small divisions = 1mW

From the graph, $V_{mp} = 1.15$ Volts

$I_{mp} = 11.8$ mA

$P_{max} = 13.8$ mW

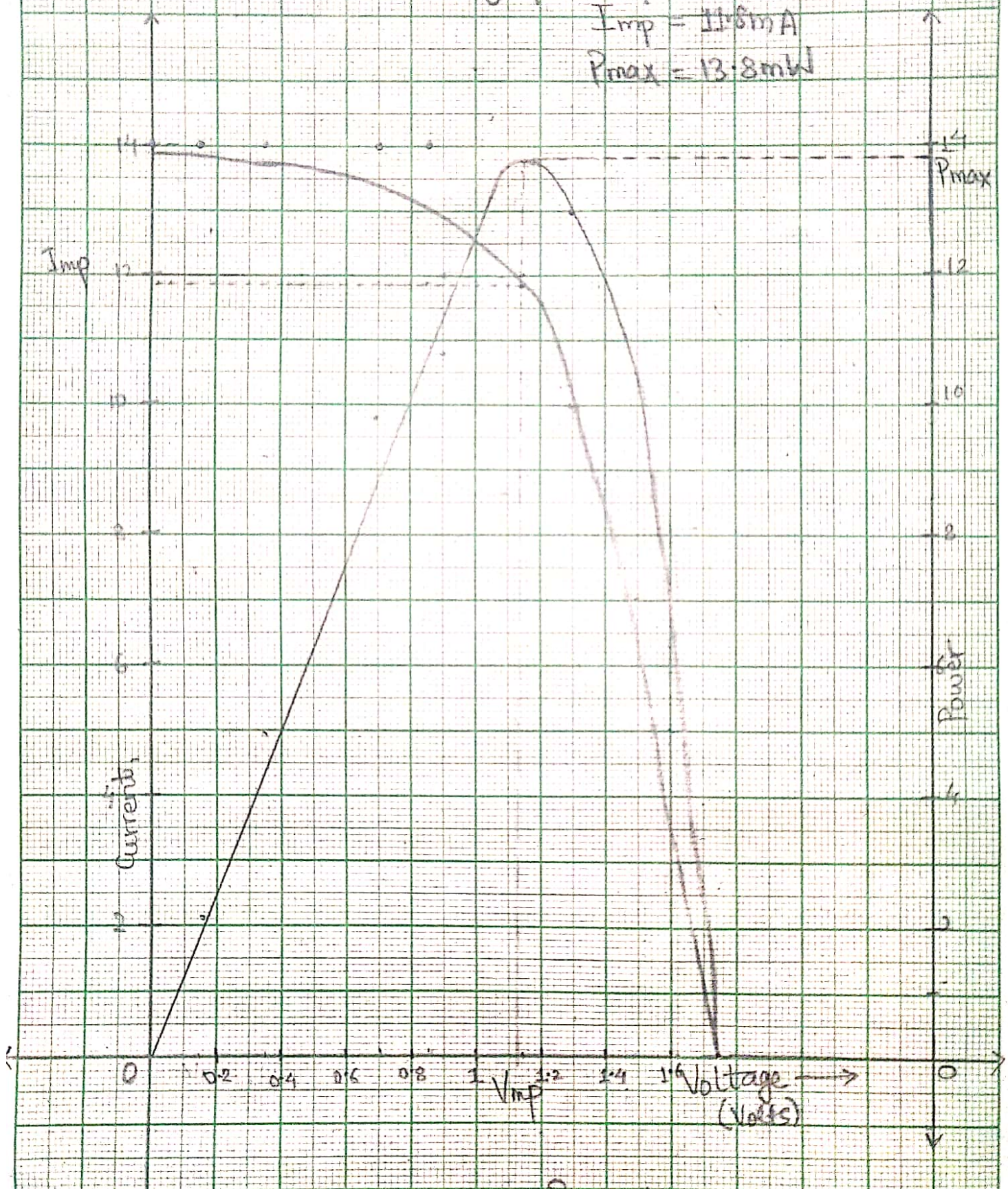

Graph:- Variation of I and P with V .